

Nyquist-Rate D/A Converters

劉 尙 大 教 授

전 자 공 학 부

Kyungpook National University

Integrated Systems Lab, Kyungpook National University



Nyquist-Rate CMOS D/A Converters

- Decoder-based DAC.
- Binary-scaled DAC.
- Thermometer-code DAC.
- Hybrid DAC.
- Oversampling DAC.

Integrated Systems Lab, Kyungpook National University



Decoder-Based D/A Converters

- ❑ Create 2^N reference signals using resistor strings.
- ❑ Pass the appropriate reference signals to the output through switches by the digital input.
- ❑ Resistor-string D/A converters.
- ❑ Folded resistor-string D/A converters.
- ❑ Multiple R-string D/A converters.




Resistor-String D/A Converters


- ❑ One of the first integrated MOS 8-bit DAC.
- ❑ Switch = pass transistor or CMOS transmission gate.
- ❑ Accuracy \Leftarrow matching precision of R
Polysilicon resistor $\Rightarrow 20 \sim 30 \Omega/\square$, 10-bit accuracy.
- ❑ Guaranteed monotonicity for voltage-insensitive V_{OS} of the buffer.
- ❑ Delay through the switch network: $\tau \approx RCn^2/2 = \sum R_{oi}C_i$.
- ❑ Tree decoding or digital decoding (2^N junctions on the output line).



 □ Resistor-string 3-bit D/A converter with tree decoding.




 □ Resistor-string 3-bit D/A converter with digital decoding.



Delay through Switch Network or Resistor String

 - Estimating the time constant for n resistors and capacitors



- Open-circuit time-constant approach ($v_i = 0$)

$$\tau \approx \sum_{i=1}^n R_{oi} C_i = RC + 2RC + \dots + nRC = \frac{n(n+1)RC}{2} \simeq \frac{n^2}{2} RC$$

- Output voltage: settling time $t_s = 7\tau$ for v_o to equal 0.999 V

$$v_i = u(t), \quad v_o \simeq 1 - e^{-t/\tau}$$




Folded Resistor-String Converters

- Decoding similar to that for a digital memory:
word lines, bit lines.
- Reduction in digital decoding area.
- Reduction of capacitive loading.
- Number of transistor junctions on the output line = $2\sqrt{2^N}$.
- Increase in speed.
- Guaranteed monotonicity for voltage-insensitive V_{OS} .



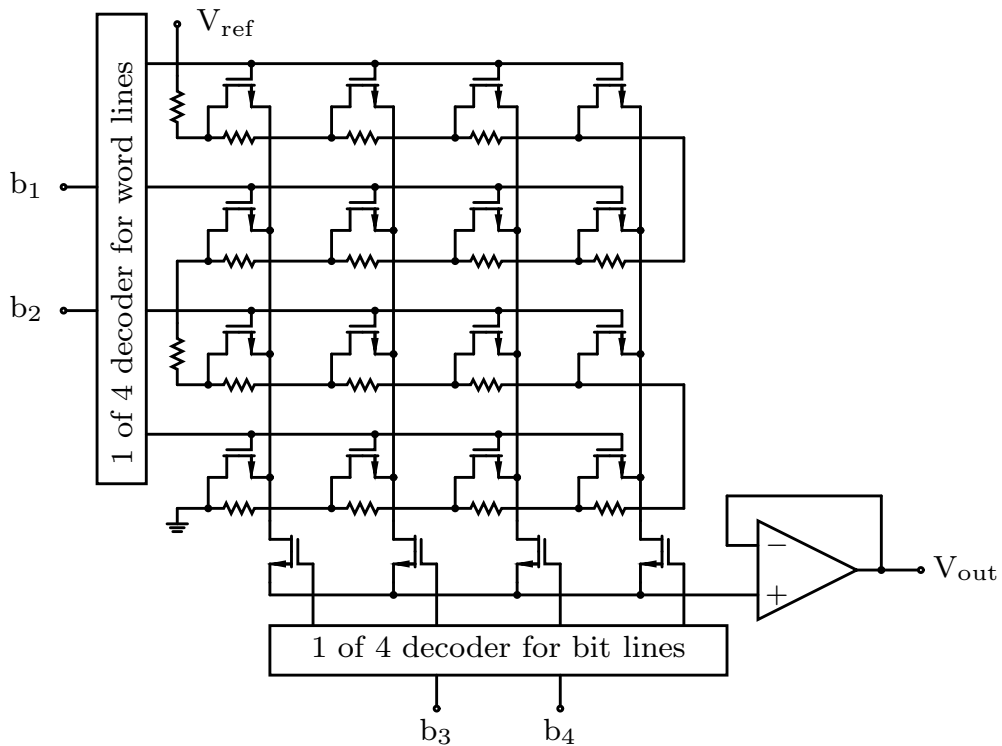- A 4-bit folded resistor-string D/A converters.



Multiple R-String Converters

- Number of resistors = $2 \times 2^{N/2} < 2^N$.
- Higher-resolution and low-power applications.
- The second resistor string linearly interpolates between the two adjacent voltages from the first resistor string.
- Not-severe matching requirements for the second resistor string (lower-order bits).
- Extra logic to make the top buffer has the higher voltage.
- Guaranteed monotonicity for matched opamps and voltage-insensitive V_{OS} .




Binary-Weighted Resistor Converters

- ❑ Popular for bipolar technology.
- ❑ Number of resistors = $N \ll 2^N$.
- ❑ Large resistance and current ratios = 2^N .
- ❑ Scaled switches for large current ratios.
- ❑ No guarantee of monotonicity.
- ❑ Glitches in high-speed operation.

$$V_{\text{out}} = -R_f V_{\text{ref}} \left(-\frac{b_1}{2R} - \frac{b_2}{4R} - \frac{b_3}{8R} - \frac{b_4}{16R} \right) = \frac{R_f}{R} V_{\text{ref}} B_{\text{in}}$$



 - ❑ Binary-weighted 4-bit resistor D/A converters.




R-2R-Based Converters

- ❑ Very popular architecture.
- ❑ Binary-weighted currents by R-2R ladder.
- ❑ Number of resistors = $2N \ll 2^N$.
- ❑ Small resistance ratio = $2 \ll 2^N$: independent of N.
- ❑ $R = 2 \sim 10 \text{ k}\Omega$, $2R = R + R$ to improve matching.
- ❑ Scaled switches for large current ratios: $1/2 \sim 1/2^N$.




- ❑ Current-driven converter: inverted R-2R ladder.
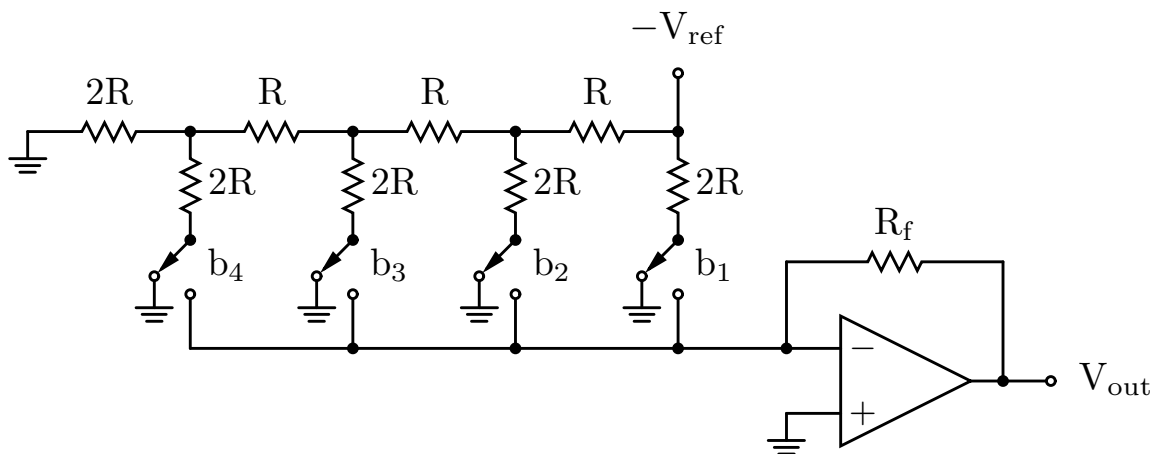
$$V_{\text{out}} = -R_f \frac{V_{\text{ref}}}{R} \left(-\frac{b_1}{2} - \frac{b_2}{4} - \frac{b_3}{8} - \frac{b_4}{16} \right) = \frac{R_f}{R} V_{\text{ref}} B_{\text{in}}$$



□ Voltage-driven converter: 4-bit R-2R based DAC.
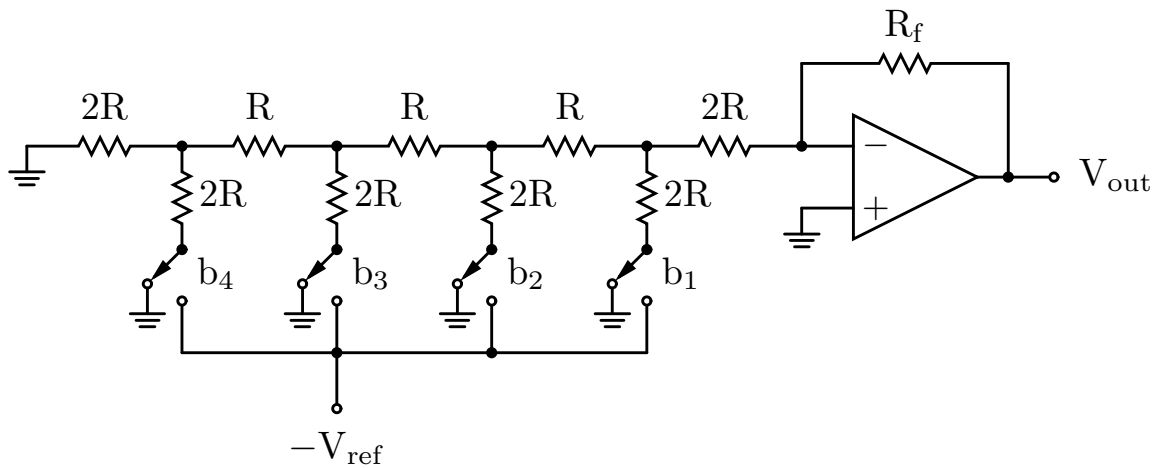
$$V_{out} = -R_f \frac{V_{ref}}{3R} \left(-\frac{b_1}{2} - \frac{b_2}{4} - \frac{b_3}{8} - \frac{b_4}{16} \right) = \frac{R_f}{3R} V_{ref} B_{in}$$




Switched-Capacitor D/A Converters

- SC gain amplifier + programmable capacitor array (PCA)
- Weighted-capacitor DAC: $V_{out} \propto V_{ref} B_{in} \rightarrow V_{in} B_{in}$ (multiplying).
- Insensitive to offset voltage, $1/f$ noise, and finite gain.
- Two $(N/2)$ -bit PCAs for large N : requires an extra opamp.
- Bottom plate never be connected to the inverting input of opamp.
- PCA programming time to reduce noise: when no potentials are altered by switching, or no signals are being processed.
- PCA connection method for easy compensation: a constant capacitive load at the input terminal of the opamp.




- Binary-array charge-redistribution D/A converter.
- Noninverting (inverting), capacitive-reset gain (C_3), deglitching capacitor (C_4) for continuous-time feedback (all switches open).
 
$$C(V_{\text{ref}} - V_{\text{OS}}) - 16CV_{\text{OS}} = -CV_{\text{OS}} + 16C(V_{\text{out}} - V_{\text{OS}}), \quad \therefore V_{\text{out}} = \frac{1}{16}V_{\text{ref}}$$



- C-2C ladder D/A converter.

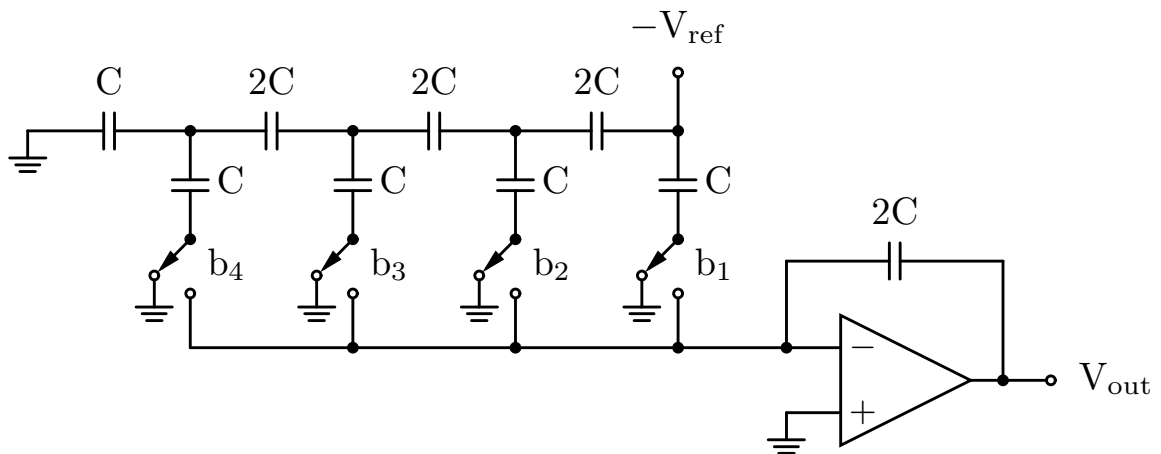

Thermometer-Code Converters

- ❑ Thermometer code: difference in one bit from next codes.
- ❑ Not a minimal representation: $2^N - 1$ bits for 2^N digital values.
- ❑ Low DNL errors: output change by only 1 LSB.
- ❑ Guaranteed monotonicity: never-lower output change.
- ❑ Reduced glitching noise:
when the input code changes from $011 \cdots 11$ to $100 \cdots 00$.
- ❑ Same area of the analog circuitry as binary-weighted approach: since the area of resistors is proportional to their size.
- ❑ All equal-size switches since they pass equal currents.




- ❑ Thermometer codes for 3-bit binary values.


| Decimal | Binary | Thermometer code |
|---------|---------------|-------------------------------|
| 0 | 000 | 0 0 0 0 0 0 0 |
| 1 | 001 | 0 0 0 0 0 0 1 |
| 2 | 010 | 0 0 0 0 0 1 1 |
| 3 | 011 | 0 0 0 0 1 1 1 |
| 4 | 100 | 0 0 0 1 1 1 1 |
| 5 | 101 | 0 0 1 1 1 1 1 |
| 6 | 110 | 0 1 1 1 1 1 1 |
| 7 | 111 | 1 1 1 1 1 1 1 |
| digits | $b_1 b_2 b_3$ | $t_1 t_2 t_3 t_4 t_5 t_6 t_7$ |



 □ A 3-bit thermometer-based D/A converter.



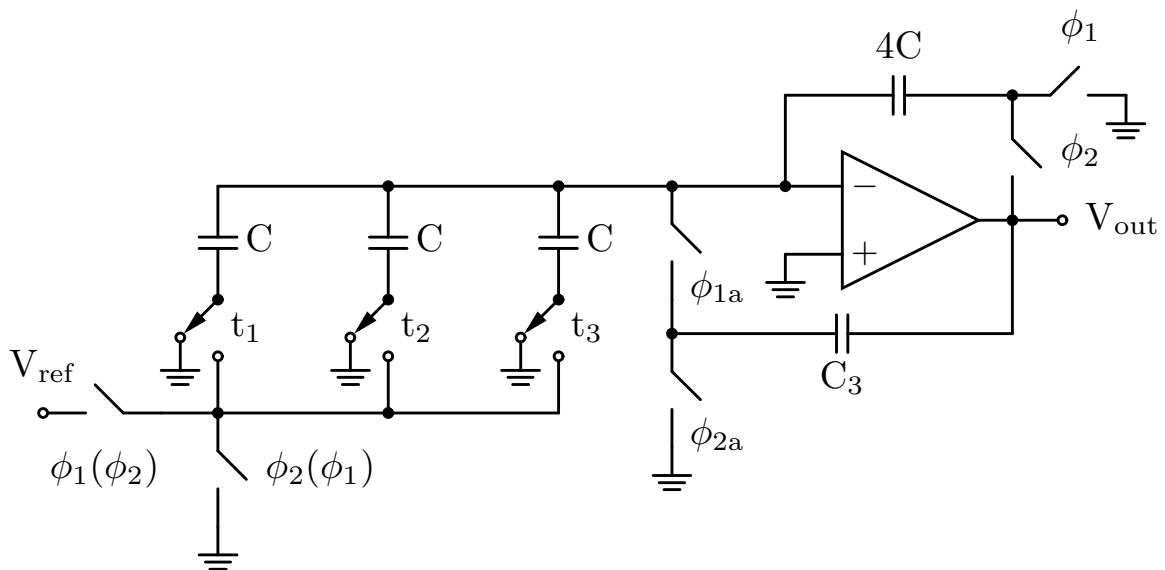□ A 2-bit thermometer-code charge-redistribution D/A converter.




Thermometer-Code Current-Mode Converters

- ❑ Basis for a variety of designs.
- ❑ Matrix current sources with equal value.
- ❑ Thermometer-code decoders for row and column decoding.
- ❑ Off-chip $50\ \Omega$ or $75\ \Omega$ load for high speed.
- ❑ Inherent monotonicity.
- ❑ Low DNL errors.
- ❑ Need for precise timing



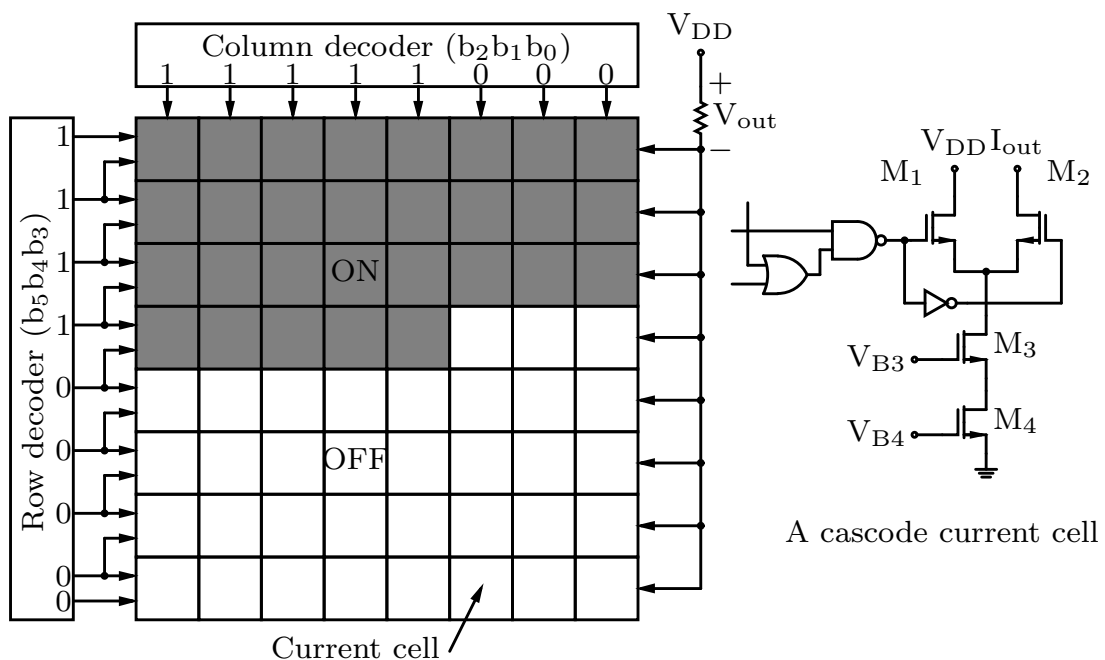- ❑ A 6-bit thermometer-code current-mode D/A converter.



Hybrid Converters

- ❑ Extremely popular approach.
- ❑ Reduced glitching and accuracy requirements in the LSBs.
- ❑ Combining the advantages of different approaches.
- ❑ Thermometer code for few MSBs + binary code for lower LSBs.
- ❑ Reduced glitching, high accuracy, saved chip area.
- ❑ Resistor-capacitor hybrid converters.
- ❑ Segmented converters.



Resistor-Capacitor Hybrid Converters

- ❑ Resistor-string DAC + SC binary-scaled DAC.
- ❑ Interpolation between the pair of voltages
by connecting the capacitors associated with a bit 1 to the higher voltage and the capacitors associated with a bit 0 to the lower voltage.


$$V_{\text{out}} = V_i + B_{\text{LSB}}(V_{i+1} - V_i) = (1 - B_{\text{LSB}})V_i + B_{\text{LSB}}V_{i+1}$$

$$V_{\text{out}} = 2^{-3}V_i + B'_{\text{LSB}}V_i + B_{\text{LSB}}V_{i+1} \quad (3\text{-bit LSB})$$

- ❑ 15-bit monotonicity without trimming.
- ❑ Very low power of 10 mW for 100 kHz conversion frequency.
- ❑ 3-bit resistor string + 3-bit binary-weighted PCA.



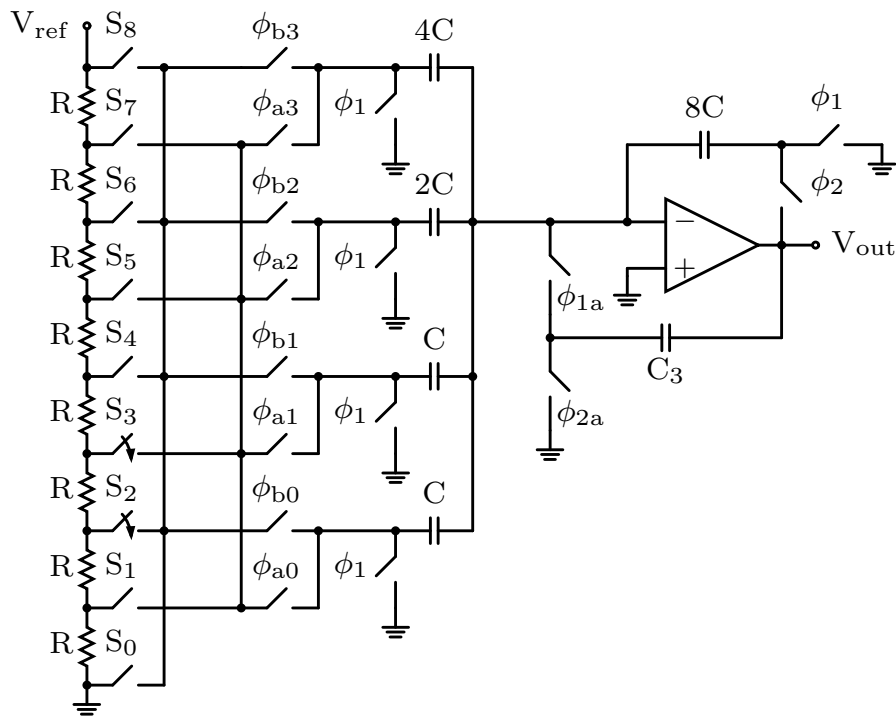□ A 6-bit resistor-capacitor hybrid D/A converter.




Segmented Converters

- The most popular design approach for D/A converters.
- Thermometer-code segment for few MSBs + binary-code segment for lower LSBs.
- The use of thermometer code for the MSB currents greatly minimizes glitches.
- One additional current source from the MSB segment is divided into binary-weighted currents of the LSB segment.
- Currents for high bits are switched to the output whereas low bits to ground.



□ A 6-bit segmented D/A converter.

 

Homework

- Simulate the 2-bit binary-array charge-redistribution D/A converter. When the input code changes as follows: 00 01 10 11 10 01 00, plot the output waveform.
- Problems 12.2, 12.4, 12.11, 12.12, 12.17.

References

- [1] Y. Nakamura, T. Miki, A. Maeda, H. Kondoh, and N. Yazawa, "A 10-b 70-MS/s CMOS D/A converter", *IEEE J. of Solid-State Circuits*, vol. 26, no. 4, pp. 637–642, 1991.
- [2] A. van den Bosch, M.A.F Borremans, M.S.J. Steyaert, W. Sansen, "A 10-bit 1-GSample/s Nyquist current-steering CMOS D/A converter", *IEEE J. of Solid-State Circuits*, vol. 36, no. 3, pp. 315–324, 2001.

