

CAD and Circuit Simulators

劉 尙 大 教 授

전 자 공 학 부

Kyungpook National University

Integrated Systems Lab, Kyungpook National University



Computer Aided Design (CAD)

- ❑ **Design** = key word
- ❑ A **working chip** NOT just a working program
- ❑ **Evolutionary** not revolutionary
- ❑ Close coupling with designers
- ❑ 20 lines of bug-free code per day

Integrated Systems Lab, Kyungpook National University



CAD Areas for Integrated Circuits

- ❑ Design verification
 - Simulation: circuit, logic, mixed
 - Functional verification
 - Timing verification
 - Physical verification
- ❑ Circuit synthesis
 - High-level synthesis
 - Combinational logic optimization
 - Sequential logic optimization
 - Layout synthesis
 - Analog circuit synthesis




- ❑ Circuit testing
 - Fault simulation
 - Automatic test pattern generation
 - Sequential test
 - Built-in self test (BIST)
 - Analog test
- ❑ Design representation
 - Domain: behavioral, structural, physical
 - Digital HDL: VHDL, ELLA, Verilog HDL, Hardware C
 - Analog HDL: VHDL-AMS, AnaVHDL, AHDL, Verilog-A
 - Design database



Circuit Simulators

 - ❑ Spice: Simulation Program with Integrated Circuit Emphasis
 - a general-purpose circuit simulator
 - *de facto* industrial standard for computer-aided circuit analysis
 - Spice2g6 (1980), Spice3f5 (1994), PSpice (1984), HSpice
- ❑ Simulation flow



- ❑ Output postprocessing using probe



Analysis Types of Spice

- ❑ DC analysis
 - operating point (.op)
 - dc sweep (.dc)
 - small-signal transfer function (.tf)
 - small-signal sensitivity (.sens)
- ❑ Transient analysis
 - time domain response (.tran)
 - Fourier analysis (.four)
- ❑ AC analysis
 - small-signal frequency response (.ac)
 - noise analysis (.noise)



Spice Input File

□ Circuit file format

```


Title statement
  Analysis requests
  Output requests
  Circuit description
    Power supplies
    Signal sources
    Element descriptions
    Model statements
+   Continued line
*   Comment line
.end

```



A Diode Circuit

□ Circuit diagram

 

□ Node number: 0 for the ground node, 1 to 9999



Example of Circuit File

❑ diode.cir

```
A diode circuit
.options reltol=0.001, abstol=1pA, vntol=1uV
.dc vI 0 1v 0.01v
.print dc v(2) (.probe)
*      step  stop  start  max
*.tran 0.01m 4m    0m    0.001m
vI 1 0 dc 1v ac 1v 0
+     sin (0v 5v 1kHz 0s 0)
D1 1 2 D1N4184
RL 2 0 1k
.model D1N4184 D (Is=0.1p Rs=16 Cjo=2p Tt=12n Bv=100)
.end
```

❑ PSpice: File->Open, File->Run Probe, Trace->Add



Basic Concepts of Circuit Simulators

- ❑ Reliable device models
- ❑ Systematic formulation
- ❑ Solution by Newton-Raphson method
- ❑ Sparse matrix techniques
- ❑ Circuit analysis methods
 - Sparse Tableau Analysis (STA): ASTAP
 - Modified Nodal Analysis (MNA): SPICE
- ❑ Stable integration formulae
- ❑ Automatic stepsize control



Sparse Tableau Analysis

□ KCL equations

$$\mathbf{A}\mathbf{i} = \mathbf{0}, \quad \mathbf{A} = \text{incidence matrix}$$

$$a_{ij} = +1 \text{ if node } i \text{ is the positive node of branch } j$$

$$\mathbf{i} = \text{branch current vector}$$

□ KVL equations

$$\mathbf{e} - \mathbf{A}^t \mathbf{v} = \mathbf{0}$$

$$\mathbf{e} = \text{branch voltage vector}$$

$$\mathbf{v} = \text{node voltage vector}$$

□ Branch equations

$$\mathbf{Z}_b \mathbf{i} - \mathbf{Y}_b \mathbf{e} = \mathbf{S} = \text{source vector}$$



□ STA equations

$$\begin{bmatrix} \mathbf{A} & \mathbf{0} & \mathbf{0} \\ \mathbf{0} & \mathbf{1} & -\mathbf{A}^t \\ \mathbf{Z}_b & -\mathbf{Y}_b & \mathbf{0} \end{bmatrix} \begin{bmatrix} \mathbf{i} \\ \mathbf{e} \\ \mathbf{v} \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \\ \mathbf{S} \end{bmatrix}$$

□ Features

- Application to **any** circuit
- Assembly by **inspection**
- **Sparse** coefficient matrix
- Sophisticated programing
- Solutions to all node voltages, all branch voltages, and all branch currents → large matrix size



Modified Nodal Analysis

- KCL equations: node equations

$$\mathbf{Y}\mathbf{v} = \mathbf{I}_s = \text{current source vector}$$

$$\mathbf{Y} = \text{node admittance matrix}$$

$$\mathbf{v} = \text{node voltage vector}$$

- KVL equations for voltage sources

- MNA equations

$$\begin{bmatrix} \mathbf{Y} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{v} \\ \mathbf{i} \end{bmatrix} = \begin{bmatrix} \mathbf{J} \\ \mathbf{E} \end{bmatrix}$$



- Features

- Application to **any** circuit
- Assembly by **inspection**
- **Sparse** coefficient matrix
- **Closeness** to \mathbf{Y} of nodal analysis: most nonzero diagonal entries
- Solutions to all node voltages and currents of voltage sources

- Example: the linear resistive circuit

1. Write KCL at the nodes

$$\textcircled{1}: i_1 + i_2 + i_3 = 0, \quad \textcircled{2}: -i_3 + i_4 - i_5 - i_6 = 0$$

$$\textcircled{3}: i_6 + i_8 = 0, \quad \textcircled{4}: i_7 - i_8 = 0$$

2. Substitute branch currents and voltages with node voltages



$$\textcircled{1}: v_1/R_1 + G_2(v_1 - v_2) + (v_1 - v_2)/R_3 = 0$$

$$\textcircled{2}: -(v_1 - v_2)/R_3 + v_2/R_4 - i_6 = I_{S5}$$

$$\textcircled{3}: i_6 + (v_3 - v_4)/R_8 = 0, \quad \textcircled{4}: i_7 - (v_3 - v_4)/R_8 = 0$$

3. Append the branch equations of branch voltage sources

- Branch 6: $v_3 - v_2 = E_{S6}$

- Branch 7: $v_4 - E_7(v_1 - v_2) = 0$

4. MNA equations


$$\begin{bmatrix} \frac{1}{R_1} + G_2 + \frac{1}{R_3} & -G_2 - \frac{1}{R_3} & 0 & 0 & 0 & 0 \\ & -\frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} & 0 & 0 & -1 & 0 \\ & 0 & 0 & \frac{1}{R_8} & -\frac{1}{R_8} & 1 & 0 \\ & 0 & 0 & -\frac{1}{R_8} & \frac{1}{R_8} & 0 & 1 \\ & 0 & -1 & 1 & 0 & 0 & 0 \\ -E_7 & E_7 & 0 & 1 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ i_6 \\ i_7 \end{bmatrix} = \begin{bmatrix} 0 \\ I_{S5} \\ 0 \\ 0 \\ E_{S6} \\ 0 \end{bmatrix}$$



MN Formulation by Inspection

□ Node-by-node (person), element-by-element (computer) basis

 □ KCL equations for a conductance element






node j : $\dots + i \dots = \dots + yv_j - yv_k \dots = \dots$

node k : $\dots - i \dots = \dots - yv_j + yv_k \dots = \dots$




□ Element stamps: row (node current), column (node voltage)
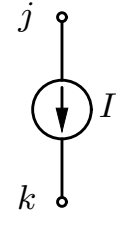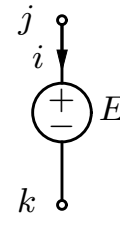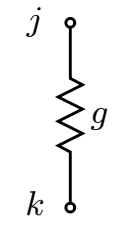
$$\begin{matrix} j \\ k \end{matrix} \begin{bmatrix} y & -y \\ -y & y \end{bmatrix}$$



Element	Symbol	Matrix	Equation
Current source		$j \begin{bmatrix} -I \\ I \end{bmatrix}$ Source vector	$i_j = I$ $i_k = -I$
Voltage source		$j \begin{matrix} j & k & l \\ \begin{bmatrix} & & 1 \\ & -1 & \\ 1 & -1 & \end{bmatrix} \end{matrix} \begin{bmatrix} \\ \\ E \end{bmatrix}$ Source vector	$i_j = i$ $i_k = -i$ $v_j - v_k = E$
Admittance		$j \begin{matrix} j & k \\ \begin{bmatrix} g & -g \\ -g & g \end{bmatrix} \end{matrix}$	$i_j = gv_{jk}$ $i_k = -gv_{jk}$

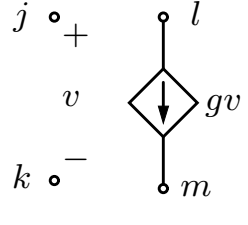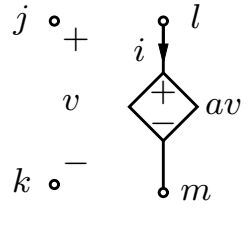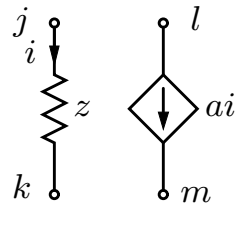

Element	Symbol	Matrix	Equation
VCCS		$l \begin{matrix} j & k \\ \begin{bmatrix} g & -g \\ -g & g \end{bmatrix} \end{matrix}$	$i_l = gv_{jk}$ $i_m = -gv_{jk}$
VCVS		$l \begin{matrix} j & k & l & m & n \\ \begin{bmatrix} & & & & 1 \\ & & & & -1 \\ -a & a & 1 & -1 \end{bmatrix} \end{matrix}$	$i_l = i$ $i_m = -i$ $v_{lm} = av_{jk}$
CCCS		$j \begin{matrix} j & k & l & m & n \\ \begin{bmatrix} & & & & 1 \\ & & & & -1 \\ & & & a & \\ & & & -a & \\ 1 & -1 & & -z \end{bmatrix} \end{matrix}$	$i_j = -i_k = i$ $i_l = -i_m = ai$ $v_j - v_k = zi$



Algorithms for Solving Linear Equations

□ Equation

$$\mathbf{Ax} = \mathbf{b}$$

□ Methods

- Iterative methods: Gauss-Jacobi, Gauss-Seidel, SOR
- Direct methods: Gaussian elimination, LU decomposition

□ Gauss-Jacobi method

$$\mathbf{Ax} = (\mathbf{L} + \mathbf{D} + \mathbf{U})\mathbf{x} = \mathbf{b}$$

$$\mathbf{D}\mathbf{x}^{k+1} = \mathbf{b} - (\mathbf{L} + \mathbf{U})\mathbf{x}^k$$



□ Example for solving a matrix equation

$$\begin{bmatrix} 4 & 1 & 2 \\ 1 & 3 & 1 \\ 1 & 2 & 5 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} 16 \\ 10 \\ 12 \end{bmatrix} \quad (1)$$

$$\mathbf{x}^0 = [0 \ 0 \ 0]^t$$

$$\mathbf{x}^1 = [4 \ 10/3 \ 12/5]^t$$

$$\mathbf{x}^2 = [59/30 \ 18/15 \ 4/15]^t$$

$$\mathbf{x}^3 = [107/30 \ 233/90 \ 229/150]^t$$

□ Gauss-Seidel method

$$(\mathbf{L} + \mathbf{D})\mathbf{x}^{k+1} = \mathbf{b} - \mathbf{U}\mathbf{x}^k$$



□ Gaussian elimination: backward substitution

$$\begin{bmatrix} a_{11} & a_{12} & \cdots & a_{1n} \\ a_{21} & a_{22} & \cdots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ a_{n1} & a_{n2} & \cdots & a_{nn} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_n \end{bmatrix}$$

$$\begin{bmatrix} a_{11} & a_{12} & \cdots & a_{1n} \\ 0 & a_{22} & \cdots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \cdots & a_{nn} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix} = \begin{bmatrix} b'_1 \\ b'_2 \\ \vdots \\ b'_n \end{bmatrix}$$

□ LU decomposition: forward, backward substitution

$$\mathbf{Ax} = \mathbf{LUx} \equiv \mathbf{Ly} = \mathbf{b}$$



$$\begin{bmatrix} a_{11} & a_{12} & \cdots & a_{1n} \\ a_{21} & a_{22} & \cdots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ a_{n1} & a_{n2} & \cdots & a_{nn} \end{bmatrix} = \begin{bmatrix} l_{11} & 0 & \cdots & 0 \\ l_{21} & l_{22} & \cdots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ l_{n1} & l_{n2} & \cdots & l_{nn} \end{bmatrix} \begin{bmatrix} u_{11} & u_{12} & \cdots & u_{1n} \\ 0 & u_{22} & \cdots & u_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \cdots & u_{nn} \end{bmatrix}$$

□ Pivoting: interchanging rows and/or columns to bring a nonzero element in diagonal element for solution accuracy

□ Exploiting sparsity

$$\text{CPU time : } O(n^3) \rightarrow O(n^{1.2})$$

$$\text{Memory : } O(n^2) \rightarrow O(n)$$



Sparse Matrix Package

```
/*
 * sparse.c
 * Test routine for the sparse matrix package
 *
 * Author:
 *   Prof. Yu Sang Dae
 *   Kyungpook National University
 *
 * Emphasis is on demonstrating how to use the basic capability of
 * the matrix routines.
 */

#include <stdio.h>
#include <math.h>
#include <sys/types.h>
#include "spconfig.h"
```



```
#include "spmatrix.h"
#include "spdefs.h"
#include "sperror.h"

main( argc, argv )
int  argc;
char *argv[];
{
    char *Matrix;
    int  i, last, size, complex, error;
    double RHS[10], Solution[10], iRHS[10], iSolution[10];
    RealNumber *pElement;

    size      = 3;
    complex   = 1;

    Matrix = spCreate( size, complex, &error );
    spErrorMessage( Matrix, stdout, NULL );
    spClear( Matrix );
```



```

error = spAddComplexElement( Matrix, 1, 1, 1.0, 1.0 );
error = spAddComplexElement( Matrix, 2, 2, 1.0, 2.0 );
error = spAddComplexElement( Matrix, 3, 3, 2.0, 2.0 );
spErrorMessage( Matrix, stdout, NULL );

/* spPrint( Matrix, PrintReordered, Data, Header ) */

spPrint( Matrix, 0, 1, 0 );
error = spFactor( Matrix );

/* spPrint( Matrix, 1, 1, 0 ); */

spErrorMessage( Matrix, stdout, NULL );

RHS[1] = 1.0; RHS[2] = 1.0; RHS[3] = 1.0;
iRHS[1] = 0.0; iRHS[2] = 0.0; iRHS[3] = 0.0;

spSolve( Matrix, RHS, Solution, iRHS, iSolution );

```



```

printf( "Solution\n" );
if ( complex ) for ( i = 1; i <= size; i++)
    printf( "%-16.9g  %-16.9gj\n", Solution[i], iSolution[i]);
else for ( i = 1; i <= size; i++)
    printf( "%-16.9g\n", Solution[i]);
spDestroy( Matrix );
}

spAddComplexElement( Matrix, Row, Col, Real, Imag )
char *Matrix;
int Row, Col;
double Real, Imag;
{
    register RealNumber *pElement;
    pElement = spGetElement( Matrix, Row, Col );
    *pElement += Real;
    *(pElement + 1) += Imag;
    return spError( Matrix );
}

```



Solution of Nonlinear Algebraic Equations

- Equation

$$f(x) = 0$$

- Taylor expansion

$$f(x^*) = 0 = f(x_k) + f'(x_k)(x^* - x_k) + R(x^* - x_k)$$

- Newton method: Newton-Raphson method

$$f'(x_k)\Delta x_k = -f(x_k)$$

$$x_{k+1} = x_k + \Delta x_k = x_k - f(x_k)/f'(x_k)$$

- Convergency: if x_k is sufficiently close to the solution, the NR method has quadratic convergence.

$$\epsilon_{k+1} = |x_{k+1} - x^*| \leq \beta \epsilon_k^2$$



- Convergence criteria: relative error tolerance E_R , absolute error tolerance E_A

$$|\Delta x_k| = |x_{k+1} - x_k| < \epsilon = E_R|x_{k+1}| + E_A$$

- Global methods: convergence from almost any starting point

- Controlled NR method

$$x_{k+1} = x_k + \alpha_k \Delta x_k, \quad 0 < \alpha \leq 1$$

- Charge-up method: capacitor || nonlinear current source, inductor + nonlinear voltage source

$$\frac{dx_{n+1}}{dt} = \frac{x_{n+1} - x_n}{\Delta t}$$

- Optimization-based method

$$\text{Minimize } f = \frac{1}{2} \mathbf{F} \cdot \mathbf{F}$$



- Damping: avoiding overflow due to exponential dependency

$$\Delta x = \text{sign}(\Delta x) \frac{\ln(1 + a|\Delta x|)}{a}$$

- Source stepping algorithm
- G_{\min} stepping algorithm

- Multidimensional NR method: Jacobian matrix \mathbf{J}

$$\mathbf{J}\Delta\mathbf{x} = -\mathbf{F}, \quad J_{ij} \equiv \frac{\partial F_i}{\partial x_j}$$

- Convergency of MNR method

- \mathbf{J} is nonsingular
- \mathbf{J} is Lipschitz continuous

$$\| \mathbf{J}(\mathbf{x}^*)^{-1} [\mathbf{J}(\mathbf{x}) - \mathbf{J}(\mathbf{x}^*)] \| \leq \beta \| \mathbf{x} - \mathbf{x}^* \|$$




Stamps of Nonlinear Elements

- $\Delta x : x$ formulation

$$\mathbf{J}\Delta\mathbf{x} = -\mathbf{F} \quad : \quad \mathbf{J}_k\mathbf{x}_{k+1} = \mathbf{J}_k\mathbf{x}_k - \mathbf{F}_k$$

- Companion models: linearized equivalent circuits for nonlinear and charge-storage elements
 
$$f_1(i, v) = i - i_D(v) = 0, \quad f_2(i, v) = i + \frac{v}{R} - I_s = 0$$





Companion Model of Diodes

□ A linearized circuit for the nonlinear diode equation

$$\begin{bmatrix} 1 & -g_k \\ 1 & 1/R \end{bmatrix} \begin{bmatrix} i_{k+1} \\ v_{k+1} \end{bmatrix} = \begin{bmatrix} 1 & -g_k \\ 1 & 1/R \end{bmatrix} \begin{bmatrix} i_k \\ v_k \end{bmatrix} - \begin{bmatrix} f_{1k} \\ f_{2k} \end{bmatrix}$$
  
$$i_{k+1} = g_k v_{k+1} + i_k - g_k v_k - f_{1k} \equiv g_k v_{k+1} + I_k = -v_{k+1}/R + I_s$$



Stamps of Nonlinear Current Sources

□ i is not part of \mathbf{x} : $f_j = \dots + i(\mathbf{x}) \dots$, $f_k = \dots - i(\mathbf{x}) \dots$

	x_1	x_2	\dots	x_n	\dots	RHS
j	$\partial i / \partial x_1$	$\partial i / \partial x_2$	\dots	$\partial i / \partial x_n$	\dots	$-i(\mathbf{x})$
k	$-\partial i / \partial x_1$	$-\partial i / \partial x_2$	\dots	$-\partial i / \partial x_n$	\dots	$+i(\mathbf{x})$

□ i is part of \mathbf{x} : $f_j = \dots + i_l(\mathbf{x})$, $f_k = \dots - i_l(\mathbf{x})$, $f_l(\mathbf{x}) = i(\mathbf{x}) - i_l = 0$

	x_1	x_2	\dots	x_n	\dots	i_l	\dots	RHS
j						+1		
k						-1		
l	$\partial i / \partial x_1$	$\partial i / \partial x_2$	\dots	$\partial i / \partial x_n$	\dots	-1	\dots	$-f_l(\mathbf{x})$

□ AC analysis

$$\mathbf{YV} = (\mathbf{G} + s\mathbf{C})\mathbf{V} = \mathbf{I}$$



```
/*
 *      main.c
 *      iCADs
 *      Integrated Circuit Analysis and Design by Simulation
 *
 *      Written by Prof. Yu Sang Dae
 *      Copyright (C) 1996 Kyungpook National University.
 *      1996. 04. 17. - 1996. 08. 18 initial version.
 */

main( argc, argv )
int argc;
char *argv[];
{
    Circuit *Ckt;
    if ( argc < 2 ) {
        printf( "Usage: icads file\n" );
        exit( 1 );
    }
}
```



```
Ckt = Malloc( Circuit );
InitSystem( Ckt );
ReadFile( argv[1], Ckt );
ParseCommand( Ckt );

MakeModelTable( Ckt );
MakeSubcktTable( Ckt );
MakeFlatCircuit( Ckt );

ParseDevice( Ckt );
SetupMatrix( Ckt );
Analysis( Ckt );

FreeCircuit( Ckt );
Free( Ckt );
return( 0 );
}
```



Homework

- (1) Write MNA equations for the linear resistive circuit using element stamps.
- (2) Solve the matrix equation (1) using the given sparse matrix package.
- (3) Derive a damping equation for the diode current $i = I_s(e^{v/V_T} - 1)$.

$$\Delta v = V_T \ln(1 + \Delta v/V_T) \quad (\Delta v > 0)$$

- (4) Find the element stamp of n MOS transistors.

References

- [1] F. H. Branin et al., “ECAP II – A new electronic circuit analysis program”, *IEEE J. Solid-State Circuits*, vol. SC-6, no. 4, pp. 146–166, 1971.
- [2] L. W. Nagel and R. A. Rohrer, “Computer analysis of nonlinear circuits excluding radiation (CANCER)”, *IEEE J. Solid-State Circuits*, vol. SC-6, no. 4, pp. 166–182, 1971.



- [3] G. D. Hachtel et al., “The sparse tableau approach to network analysis and design”, *IEEE Trans. on Circuit Theory*, vol. CT-18, pp. 101–108, 1971.
- [4] C. W. Ho et al., “The modified nodal approach to network analysis”, *IEEE Trans. on Circuits and Systems*, vol. CAS-22, No. 6, pp. 504–509, 1975.
- [5] D. A. Zein, “Solution of a set of nonlinear algebraic equations for general-purpose CAD programs”, *IEEE Circuits and Devices Magazine*, vol. 1, pp. 7–20, 1985.
- [6] E. Ngoya, J. Rousset, and J. J. Obregon, “Newton-Raphson iteration speed-up algorithm for the solution of nonlinear circuit equations in general-purpose CAD programs”, *IEEE Tran. on Computer-Aided Design of Integrated Circuits and Systems*, vol. 16, pp. 638–644, 1997.
- [7] J. Vlach and K. Singhal, *Computer Methods for Circuit Analysis and Design*, Van Nostrand Reinhold, 1983.
- [8] W. J. McCalla, *Fundamentals of Computer-Aided Circuit Simulation*, Kluwer Academic Publishers, 1988.

