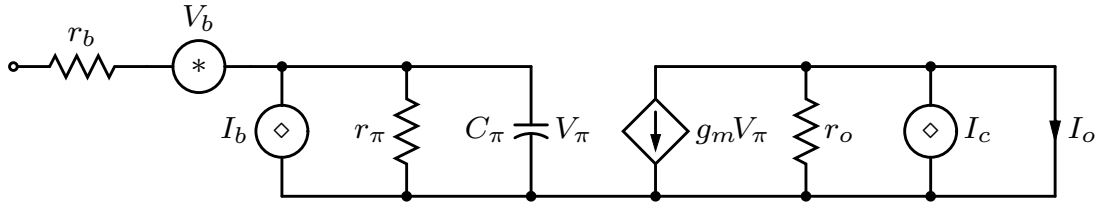


### Noise Model for Bipolar Transistors

- Bipolar transistor equivalent circuit with noise sources:  $V_b^2 = 4kTr_b$ ,  $I_c^2 = 2qI_C$ ,  $I_b^2 = 2qI_B + K_1I_B/f + K_2I_B/[1 + (f/f_c)^2]$  (burst noise)



- Equivalent input noise voltage  $V_i$ : short-circuited input,  $r_\pi \gg r_b \approx 0$ ,  $g_m = I_C/V_T$ , equivalent input noise resistance  $(r_b + 1/2g_m)$

$$I_o = g_m V_b + I_c \equiv g_m V_i \quad \rightarrow \quad V_i = V_b + \frac{I_c}{g_m}$$

$$V_i^2 = V_b^2 + \frac{I_c^2}{g_m^2} = 4kT \left( r_b + \frac{2qI_C}{4kTg_m^2} \right) = 4kT \left( r_b + \frac{1}{2g_m} \right)$$

- Equivalent input noise current  $I_i$ : open-circuited input,  $V_b$  is excluded, equivalent input shot noise current  $(I_B + K'_1I_B/f + I_C/|\beta|^2)$

$$I_o = g_m r_\pi I_b + I_c = \beta I_b + I_c \equiv \beta I_i \quad \rightarrow \quad I_i = I_b + \frac{I_c}{\beta}$$

$$I_i^2 = I_b^2 + \frac{I_c^2}{|\beta|^2} \simeq 2qI_B + \frac{K_1I_B}{f} + \frac{2qI_C}{|\beta|^2} = 2q \left( I_B + \frac{K'_1I_B}{f} + \frac{I_C}{|\beta|^2} \right)$$

$$\simeq 2q \left( I_B + \frac{I_C}{\beta_0^2} \right) \quad (\text{midband}) \quad \beta(s) = \frac{\beta_0}{1 + s/\omega_\beta} \simeq \beta_0$$

$$\simeq 2q \left( I_B + \frac{I_C f^2}{\beta_0^2 f_\beta^2} \right) \quad (f > f_c = 50 \text{ MHz}) \quad \beta(s) = \frac{\beta_0}{s/\omega_\beta}$$

$$I_B \equiv \frac{I_C f^2}{\beta_0^2 f_\beta^2} = \frac{I_C f^2}{f_T^2} \quad \text{for } f = f_c \quad \therefore f_c = \frac{f_T}{\sqrt{\beta_0}}$$

- Output noise  $V_{no1}^2$  due only to noise currents  $I_{n1}$ ,  $I_{nf}$ ,  $I_{n-}$

$$V_{no1} = I_{ni}(R_f \parallel C_f) = (I_{n1} + I_{nf} + I_{n-}) \frac{R_f/sC_f}{R_f + 1/sC_f}$$

$$V_{no1}^2 = (I_{n1}^2 + I_{nf}^2 + I_{n-}^2) R_f^2 \left| \frac{1}{1 + jf/f_0} \right|^2, \quad f_0 = \frac{1}{2\pi R_f C_f}$$

- Output noise  $V_{no2}^2$  due only to noise voltages  $V_n$ ,  $V_{n2}$ ,  $I_{n+}R_2$

$$V_{no2} = V_{ni} \left( 1 + \frac{R_f \parallel C_f}{R_1} \right) = V_{ni} \left( \frac{1 + R_f/R_1 + sR_f C_f}{1 + sR_f C_f} \right)$$


$$= V_{ni}(1 + R_f/R_1) \left( \frac{1 + sR_f C_f / (1 + R_f/R_1)}{1 + sR_f C_f} \right)$$

$$\equiv V_{ni}(1 + R_f/R_1) \left( \frac{1 + jf/f_1}{1 + jf/f_0} \right), \quad f_1 = (1 + R_f/R_1)f_0$$

$$V_{no2}^2 = (V_n^2 + V_{n2}^2 + I_{n+}^2 R_2^2) (1 + R_f/R_1)^2 \left| \frac{1 + jf/f_1}{1 + jf/f_0} \right|^2$$



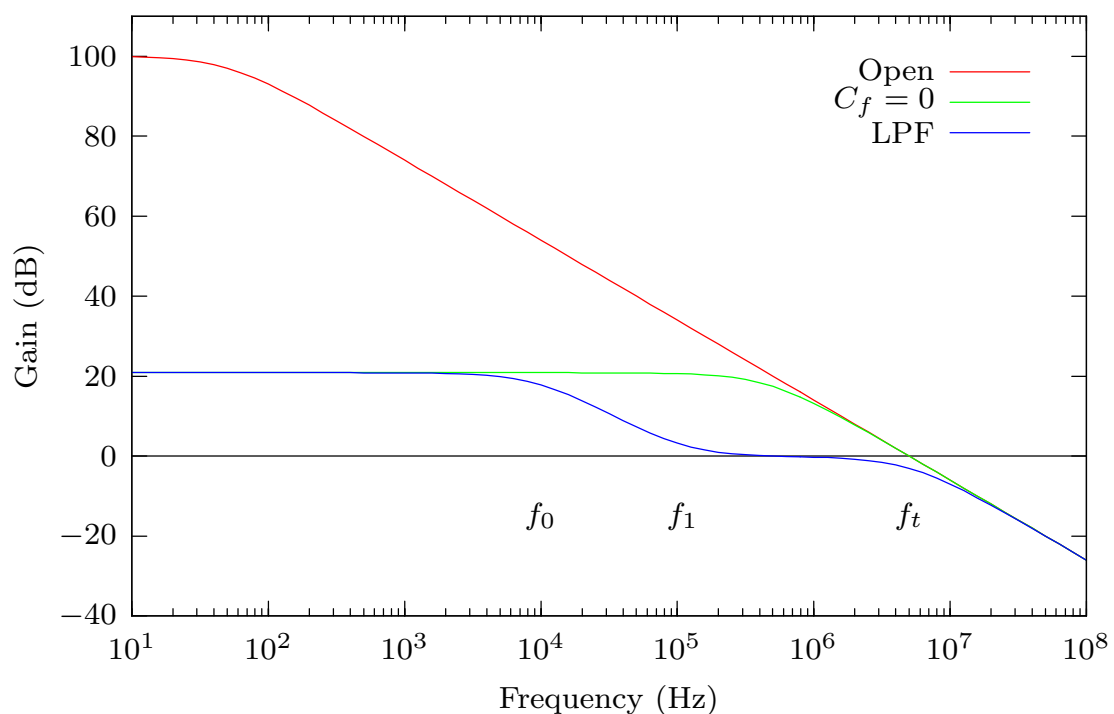- Gain responses of open-loop opamp, noninverting amp, active LPF




□ Equivalent circuit of a differential amplifier for noise analysis

$$(v_{gs1} + v_{n1} = v_{gs2} + v_{n2} = -v_s, v_d = v_{gs3} + v_{n3} = v_{gs4} + v_{n4})$$

$$g_{o5}v_s + g_{o1}(v_s - v_d) + g_{o1}(v_s - v_o) - 2g_{m1}v_{gs1} = g_{m5}v_{n5}, \quad v_{gs1} = -v_s$$

$$g_{o1}(v_d - v_s) + g_{o3}v_d + g_{m1}v_{gs1} + g_{m3}v_{gs3} = 0, \quad v_{gs3} = v_d - v_{n3}$$
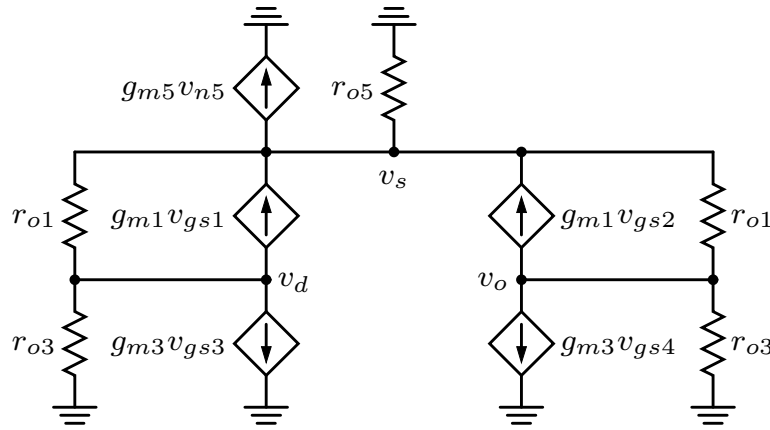
$$g_{o1}(v_o - v_s) + g_{o3}v_o + g_{m1}v_{gs2} + g_{m3}v_{gs4} = 0, \quad v_{gs4} = v_d - v_{n4}$$



□ Low-frequency noises of  $M_5$  and  $M_3$  in the differential amplifier

$$\begin{bmatrix} 2g_{m1} + 2g_{o1} + g_{o5} & -g_{o1} & -g_{o1} \\ -(g_{m1} + g_{o1}) & g_{m3} + g_{o1} + g_{o3} & 0 \\ -(g_{m1} + g_{o1}) & g_{m3} & g_{o1} + g_{o3} \end{bmatrix} \begin{bmatrix} v_s \\ v_d \\ v_o \end{bmatrix} = \begin{bmatrix} g_{m5}v_{n5} \\ g_{m3}v_{n3} \\ g_{m3}v_{n4} \end{bmatrix}$$

$$\Delta = (g_{o1} + g_{o3})[(2g_{m1} + 2g_{o1} + g_{o5})(g_{m3} + g_{o1} + g_{o3}) - 2(g_{m1} + g_{o1})g_{o1}]$$

$$\simeq (g_{o1} + g_{o3})(2g_{m1} + 2g_{o1} + g_{o5})(g_{m3} + g_{o3})$$

$$\Delta_5 = -(g_{m1} + g_{o1})g_{m3} + (g_{m1} + g_{o1})(g_{m3} + g_{o1} + g_{o3})$$

$$\therefore \frac{v_o}{v_{n5}} = \frac{g_{m5}\Delta_5}{\Delta} = \frac{g_{m5}(g_{m1} + g_{o1})(g_{o1} + g_{o3})}{\Delta} \simeq \frac{g_{m5}}{2g_{m3}}$$

$$\Delta_3 = (2g_{m1} + 2g_{o1} + g_{o5})g_{m3} - (g_{m1} + g_{o1})g_{o1}$$

$$\therefore \frac{v_o}{v_{n3}} = \frac{-g_{m3}\Delta_3}{\Delta} \simeq \frac{-g_{m3}}{g_{o1} + g_{o3}} = -g_{m3}R_o$$

