

Basic Opamp Design and Compensation

劉 尙 大 教 授

전 자 공 학 부

Kyungpook National University

Integrated Systems Lab, Kyungpook National University



CMOS Opamp Design


- ❑ Fundamental principles of basic opamp design.
- ❑ Two-stage CMOS opamp is used to illustrate these principles.
- ❑ Compensation techniques for stability when used with feedback.
- ❑ Other design techniques: $V_{OS} \rightarrow 0$, process-insensitive compensation.
- ❑ Biasing circuits of opamps with stability for power-supply voltage, process, and temperature variations.
- ❑ Advanced architectures: fully-differential opamps for better noise rejection in high-performance analog and mixed ICs.

Integrated Systems Lab, Kyungpook National University




Two-Stage CMOS Opamp

- ❑ A popular approach for both bipolar and CMOS opamps.
- ❑ An excellent example to illustrate design concepts.
- ❑ Two-stage = number of gain stages.
- ❑ Output buffer is used only when resistive loads need to be driven.
- ❑ Differential pair without body effect for better matching.
- ❑ C_C = compensation capacitor with Miller effect.
- ❑ $L = 1.5 \sim 2$ times the minimum feature size = $3 \sim 4\lambda$.

 

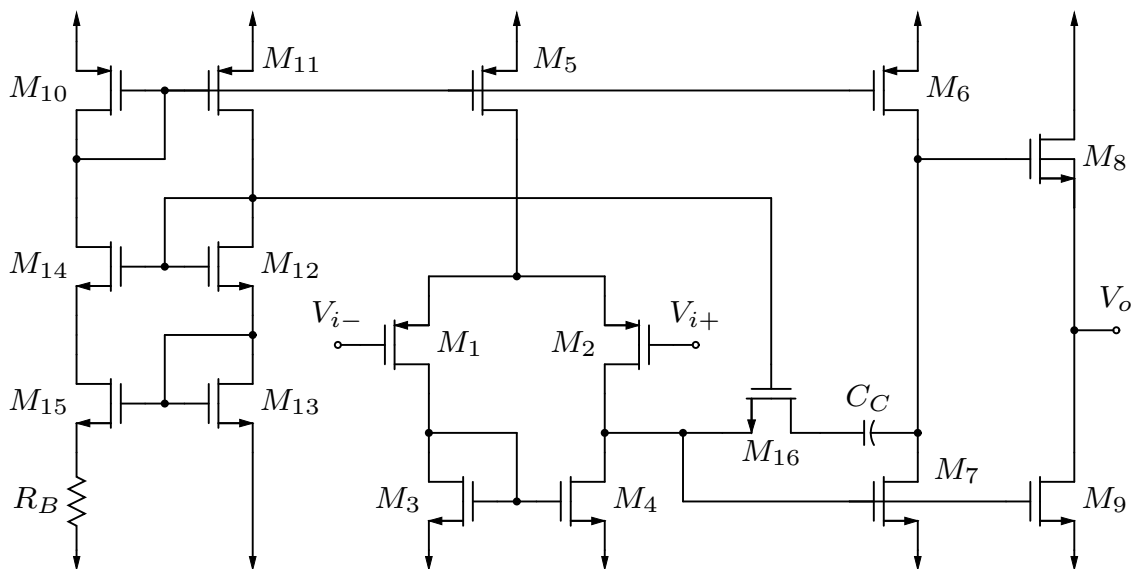- ❑ A circuit diagram of a two-stage CMOS operational amplifier.



DC Gain of Opamp

- High DC gain for high accuracy: $A_0 = A_{01}A_{02}A_{03}$
- Gain of the first stage without short-channel effects.

$$-A_{01} = g_{m1}(r_{ds2} \parallel r_{ds4}) \equiv g_{m1}R_{o1}$$

$$g_{m1} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}, \quad r_{dsi} \approx \alpha \frac{L_i}{I_{Di}} \sqrt{V_{DGi} + V_{ti}}$$

- Gain of the second stage without short-channel effects.

$$-A_{02} = g_{m7}(r_{ds6} \parallel r_{ds7}) \equiv g_{m7}R_{o2}$$

- Gain of the output buffer without body effect: load conductance G_L .

$$A_{03} \simeq \frac{g_{m8}}{g_{m8} + g_{ds8} + g_{ds9} + G_L}$$



Frequency Response of Opamp

- A simplified model: ignore all C s except C_C , and Q_{16} .
- A capacitive load on the first stage: Miller capacitance.

$$C_M = C_C(1 + A_2) \simeq C_C A_{02}$$

- Frequency response of the first stage: $\omega_{p1} \equiv 1/R_{o1}C_M$.


$$A_1 = \frac{V_1}{V_i} = -g_{m1} \left(r_{ds2} \parallel r_{ds4} \parallel \frac{1}{sC_M} \right) = \frac{-g_{m1}R_{o1}}{1 + sR_{o1}C_M}$$

- Overall frequency response and unity-gain frequency.

$$A(s) \equiv \frac{V_o}{V_i} = \frac{A_0}{1 + s/\omega_{p1}} = \frac{g_{m1}R_{o1}A_{02}A_{03}}{1 + sR_{o1}C_M} \simeq \frac{g_{m1}}{sC_C}, \quad \omega_{ta} = \frac{g_{m1}}{C_C}$$



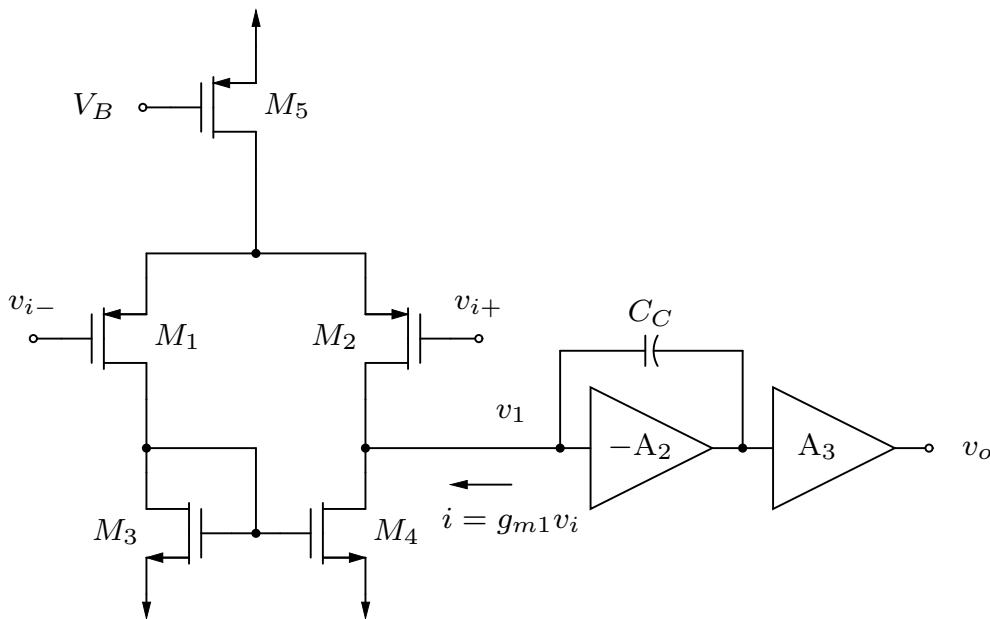□ A simplified model used to find the midband frequency response.



Slew Rate of Opamp

□ Maximum change rate of output for a large input signal.

$$\begin{aligned}
 \text{SR} &\equiv \left. \frac{dv_o}{dt} \right|_{\max} \simeq \left. \frac{dv_2}{dt} \right|_{\max} = \frac{I_{D5}}{C_C} \left(i \simeq C_C \frac{dv_2}{dt} \right) \\
 &= \frac{2I_{D1}\omega_{ta}}{g_{m1}} = V_{\text{eff1}}\omega_{ta} = \sqrt{\frac{2I_{D1}}{\mu_p C_{ox}(W/L)_1}} \omega_{ta}
 \end{aligned}$$

□ For given power dissipation and ω_{ta} , increase V_{eff1} for large SR \rightarrow lower g_{m1} ($2I_D/V_{\text{eff1}}$), dc gain, and distortion, higher thermal noise.

□ Small-signal condition, flicker and thermal noise sources.

$$v_{gs} \ll 2(V_{GS} - V_t), \quad v_g^2(f) = \frac{K}{WLC_{ox}f} + 4kT \left(\frac{2}{3} \right) \frac{1}{g_m}$$



Systematic Offset Voltage

- Design condition for minimum V_{OS} : $I_{D7} = |I_{D6}|$ for $V_{i-} = 0 = V_{i+}$.

$$\frac{I_{D6}}{I_{D5}} = \frac{(W/L)_6}{(W/L)_5} = \frac{I_{D7}}{|I_{D5}|} = \frac{I_{D7}}{2I_{D4}}, \quad V_{GS4} = V_{DS4} = V_{GS7}$$

$$\therefore \frac{(W/L)_7}{(W/L)_4} = \frac{I_{D7}}{I_{D4}} = 2 \frac{(W/L)_6}{(W/L)_5}$$


- Random offset voltage: the voltage drop of the output buffer, any mismatches between the output impedances of p and n MOSTs.

$$V_{OS} \leq 5 \text{ mV}$$

- The input and gain stages of the two-stage opamp.



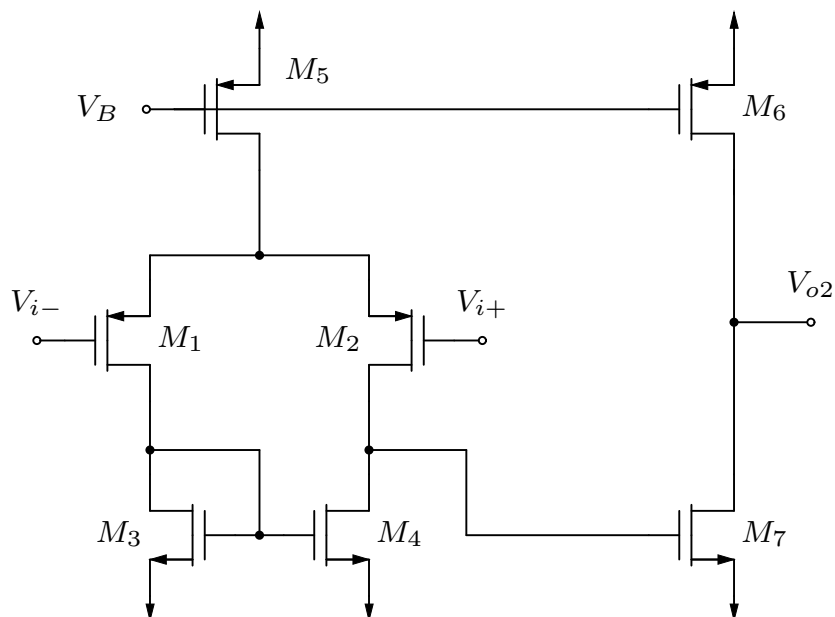- The input and gain stages of the two-stage CMOS opamp.



n-Channel or p-Channel Input Stage

- ❑ The DC gain: unaffected by the choice since both designs have one stage with nMOSTs and one stage with pMOSTs.
- ❑ The structure with pMOST input stage and the second stage with nMOS drive transistor *maximizes* slew rate and g_{m7} for high-frequency operation. ($\tan^{-1} \frac{2}{3} = 33.7^\circ$)

$$\therefore \omega_{ta} < \frac{2}{3}\omega_{p2} \text{ for } 60^\circ \text{ PM, } \omega_{p2} \propto g_{m7}$$

- ❑ An nMOST source follower will have less voltage drop V_{GS} for given I_D , less effect of load capacitance C_L on ω_{p2} due to a higher g_m , less degradation of gain for small load resistances.
- ❑ pMOSTs have less 1/f noise than nMOSTs but more thermal noise.




Feedback and Opamp Compensation

- ❑ Opamps in closed-loop configurations: should be stable at all frequencies as well as over the frequency range of interest.
- ❑ How to compensate for good stability and settling characteristics.
- ❑ Optimum compensation of opamps: one of the most difficult parts of the opamp design procedure.
- ❑ Systematic approach: near-optimum compensation.
- ❑ Stable frequency response by biasing to stabilize transconductances for power-supply voltage, process, and temperature variations.




Condition for Stability

 - The transient reponse of a stable amplifier must decrease with time.
 - ↔ The poles of A_f must lie in the open left-half s plane ($e^{\sigma_p t} e^{j\omega_p t}$).
- Nyquist criterion: Nyquist plot for loop gain $A\beta$ does not enclose $(-1, 0)$.



Gain and Phase Margins

- Bode plot for the loop gain $A\beta$

 

First-Order Model of Feedback Amplifier

- Transfer function of a dominant-pole compensated opamp.

$$A(s) = \frac{A_0}{1 + s/\omega_{p1}}$$

- Definition of the unity-gain frequency of an opamp.

$$|A(j\omega_{ta})| \equiv 1 \simeq \frac{A_0}{\omega_{ta}/\omega_{p1}}, \quad \omega_{ta} = A_0\omega_{p1}$$

- Transfer function of feedback amplifiers ($0 \leq \beta \leq 1$)

$$A_f(s) = \frac{A(s)}{1 + \beta A(s)} = \frac{1/\beta}{1 + 1/\beta A_0 + s/\beta\omega_{ta}} \simeq \frac{1/\beta}{1 + s/\beta\omega_{ta}}$$

- 3-dB frequency: $\omega_t =$ unity-gain frequency of loop gain $A\beta$.

$$\omega_{3dB} \simeq \beta\omega_{ta} \simeq \omega_t$$



Linear Settling Time

- Charge transfer within half a clock period in SC circuits.
- Settling time = nonlinear and linear settling time segments.
- Linear settling time due to finite ω_{ta} for a step input: 1% (0.1%) settling at a time of 4.6τ (7τ), $v_i(t) = V_0u(t)$, $V_i = V_0/s$

$$V_o = A_f(s)V_i = \frac{V_0/\beta}{s(1 + s/\omega_t)} = \frac{V_0}{\beta} \left(\frac{1}{s} - \frac{1}{s + \omega_t} \right)$$

$$v_o(t) = \frac{V_0}{\beta} (1 - e^{-t/\tau})u(t), \quad \tau = \frac{1}{\omega_t} = \frac{1}{\beta\omega_{ta}}$$


- Nonlinear settling time due to slew-rate limiting.

$$\text{SR} < \left. \frac{dv_o}{dt} \right|_{\max} = \frac{V_0}{\beta\tau} = \omega_{ta}V_0$$



Switched-Capacitor Amplifier

 - Amplifier with capacitive feedback during one clock phase: example 5.5



$$C_1 v_i = -C_2 v_o, \quad \frac{v_o}{v_i} = -\frac{C_1}{C_2}, \quad Z_t = \frac{1}{sC_t}, \quad C_t = \frac{C_1 C_2}{C_1 + C_2}$$

- Two port analysis: unilateral amplifier and feedback network.
- Return ratio analysis: bilateral β , the broken loop is terminated with Z_t

$$\mathcal{R} = A\beta = - \left. \frac{V_r}{V_t} \right|_{Z_t} = -\frac{V_r}{V_f} \frac{V_f}{V_t} = A \left(\frac{C_2}{C_1 + C_2} \right), \quad \omega_{ta} \geq \frac{1}{\tau\beta}$$



Opamp Compensation

- It is important to *accurately* model the transfer function at higher frequencies where the loop gain is unity.
- A model of $A(s)$ by an equivalent pole when all poles and zeros are on the real axis: $1/\omega_{eq} \simeq \sum(1/\omega_{pi}) - \sum(1/\omega_{zi})$, 5% error for $\omega_i > 2\omega_{eq}$

$$A(s) \simeq \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{eq})} \simeq \frac{\omega_{ta}}{s(1 + s/\omega_{eq})}, \quad \omega \gg \omega_{p1}$$

- The unity-gain frequency ω_t of the loop gain.

$$LG(s) \equiv \beta A(s) = \frac{\beta\omega_{ta}}{s(1 + s/\omega_{eq})}, \quad \beta\omega_{ta} = \omega_t \sqrt{1 + (\omega_t/\omega_{eq})^2}$$

- The phase margin of the loop gain.

$$PM = \angle LG(j\omega_t) - (-180^\circ) = 90^\circ - \tan^{-1}(\omega_t/\omega_{eq})$$



- The 2nd-order approximation of $A_f(s)$ near ω_t

$$A_f(s) \simeq \frac{K\omega_0^2}{s^2 + (\omega_0/Q)s + \omega_0^2}, \quad \omega_0 \simeq \sqrt{\beta\omega_{ta}\omega_{eq}}, \quad Q \simeq \sqrt{\beta\omega_{ta}/\omega_{eq}}$$

- The relationship between PM, ω_t/ω_{eq} , Q factor, overshoot, and $t_s\omega_t$

PM	ω_t/ω_{eq}	Q factor	Overshoot	$t_s\omega_t$
55°	0.700	0.925	13.3%	12.1
60°	0.580	0.817	8.7%	9.5
65°	0.470	0.717	4.7%	7.5
70°	0.360	0.622	1.4%	5.8
75°	0.270	0.527	0.008%	4.5

- PM = 80° to 85° for process and temperature variations.



Transfer Function of Two-Stage Opamp

- Small signal model of the opamp without output buffer

$$R_1 = r_{ds2} \parallel r_{ds4}, \quad C_1 = C_{db2} + C_{db4} + C_{gs7}$$

$$R_2 = r_{ds6} \parallel r_{ds7}, \quad C_2 = C_{db6} + C_{db7} + C_{L2}$$

- Transfer function by nodal analysis: $R_C = 0$, $\omega_{p1} \ll \omega_{p2}$

$$\frac{V_o}{V_i} = \frac{g_{m1}g_{m2}R_1R_2(1 + s/\omega_z)}{1 + as + bs^2}$$

$$a = g_{m7}R_1R_2C_C + R_1(C_1 + C_C) + R_2(C_2 + C_C)$$


$$b = R_1R_2(C_1C_2 + C_1C_C + C_2C_C), \quad \omega_z = -g_{m7}/C_C$$

$$1 + as + bs^2 = (1 + s/\omega_{p1})(1 + s/\omega_{p2}) \simeq 1 + s/\omega_{p1} + s^2/\omega_{p1}\omega_{p2}$$

$$\omega_{p1} = \frac{1}{a} \simeq \frac{1}{g_{m7}R_1R_2C_C}, \quad \omega_{p2} = \frac{1}{b\omega_{p1}} \simeq \frac{g_{m7}}{C_1 + C_2}$$



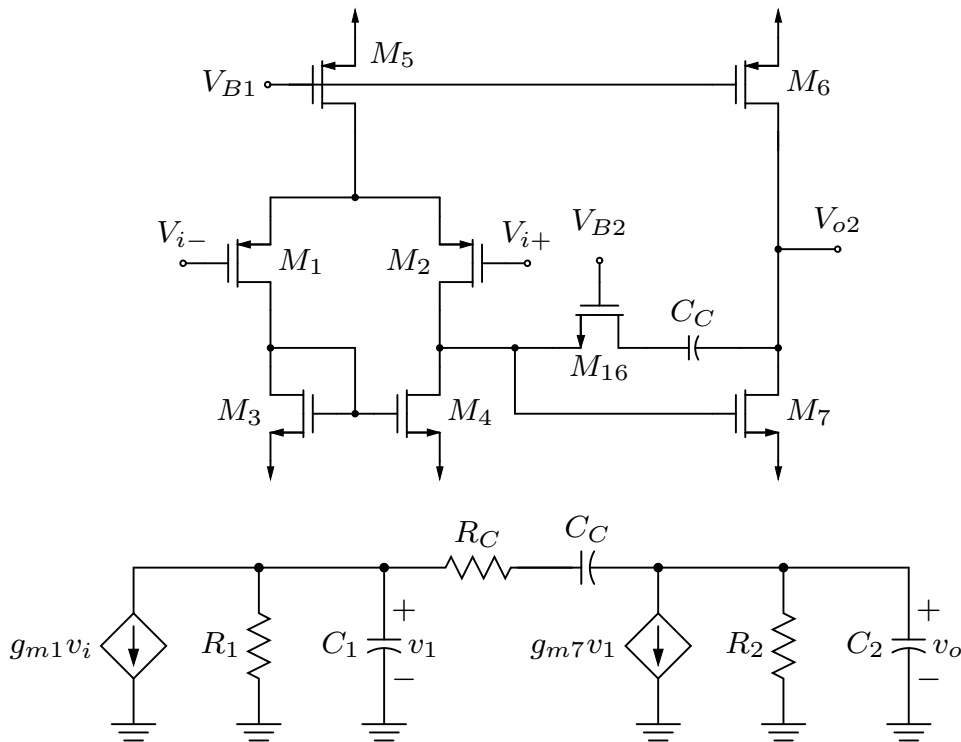□ A compensation network and a small signal model of the opamp.



Compensation of Two-Stage Opamp

- Dominant-pole compensation: controls ω_{p1} by C_C .
- Pole-splitting compensation: Miller effect, $R_C = 0$, $\omega_{p1} \ll \omega_{p2}$, RHP zero $(1 + s/\omega_z) \rightarrow$ negative phase shift $(\phi_z = \tan^{-1} \frac{\omega}{\omega_z} < 0)$

$$\omega_{p1} \simeq \frac{1}{g_{m7}R_1R_2C_C}, \quad \omega_{p2} \simeq \frac{g_{m7}}{C_1 + C_2}, \quad \omega_z = -\frac{g_{m7}}{C_C}$$

- Transistor Q_{16} as a resistor: $V_{DS16} = 0$ since $I_{D16} = 0$.

$$R_C = r_{ds16} = \frac{1}{\mu_n C_{ox}(W/L)_{16} V_{eff16}} = \frac{1}{g_{m16}}$$

- Lead compensation: $R_C > 1/g_{m7} \rightarrow \omega_z > 0$, $\phi_z > 0$

$$\frac{V_1}{R_C + 1/(-\omega_z C_C)} = g_{m7}V_1, \quad \omega_z = -\frac{1}{(1/g_{m7} - R_C)C_C}$$



Techniques of Lead Compensation

- Elimination of the RHP zero: $\omega_z = \infty$.

$$\omega_z = -\frac{1}{(1/g_{m7} - R_C)C_C}, \quad R_C = 1/g_{m7}$$

- Movement of the RHP zero into LHP to cancel ω_{p2} : $\omega_z = \omega_{p2}$.

$$R_C = \frac{1}{g_{m7}} \left(1 + \frac{C_1 + C_2}{C_C} \right)$$

- Movement of the RHP zero to $1.2\omega_t$ in LHP: almost optimum.

$$R_C \gg 1/g_{m7}, \quad \omega_z \simeq \frac{1}{R_C C_C} \simeq 1.2\omega_t, \quad R_C \simeq \frac{1}{1.2\omega_t C_C} = \frac{1}{1.2g_{m1}}$$




Design Algorithm of Two-Stage Opamp

 1. Choose arbitrarily, $C'_C \simeq 5$ pF ($R_C = 0$).
2. Find the frequency ω_t where a -135° phase shift exists, and the gain A' at this frequency using Spice $\rightarrow \omega_t = \omega_{eq}$
3. Choose a new C_C so that ω_t becomes the unity-gain frequency of the loop gain: $GB = g_{m1}/C'_C = A'g_{m1}/C_C \rightarrow C_C = A'C'_C$
4. Choose $R_C = 1/1.2\omega_t C_C$ for $PM \simeq 85^\circ$. One should check *frequency doublets* of pole-zero pairs which may cause severe degradation of settling time. $\phi(j\omega_t) = -\angle \frac{\omega_t}{\omega_{p1}} - \angle \frac{\omega_t}{\omega_{eq}} + \angle \frac{\omega_t}{\omega_z} = -90 - 45 + 40 = -95^\circ$
5. Increase C_C if the phase margin is not adequate.
6. Replace R_C by a transistor, and tune the device sizes using Spice.



- Relationship between phase margin and settling time for channel widths of M_{16}



Compensation Independent of Process and T

- Relative positions of pole and zero: $\omega_t/\omega_z \propto (g_{m1}/g_{m7})(g_{m7}R_C - 1)$

$$\omega_t = \frac{g_{m1}}{C_C}, \quad \omega_{p2} \simeq \frac{g_{m7}}{C_1 + C_2}, \quad \omega_z = -\frac{1}{(1/g_{m7} - R_C)C_C}$$

- Constant ratios of capacitances by gate oxides.
- Constant ratios of transconductances by the same bias network.

$$\frac{I_{D7}}{I_{D13}} = \frac{(W/L)_6}{(W/L)_{11}} \equiv \frac{(W/L)_7}{(W/L)_{13}} \text{ (design rule)} \rightarrow \frac{V_{\text{eff}7}}{V_{\text{eff}16}} \stackrel{\textcircled{1}}{=} \frac{V_{\text{eff}13}}{V_{\text{eff}12}}$$

$$(g_m = \mu_n C_{ox} (W/L) V_{\text{eff}}, \quad I_{D12} \stackrel{\textcircled{3}}{=} I_{D13})$$

$$\therefore g_{m7}R_C = \frac{g_{m7}}{g_{m16}} = \frac{(W/L)_7 V_{\text{eff}7}}{(W/L)_{16} V_{\text{eff}16}} = \frac{(W/L)_7}{(W/L)_{16}} \sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}}$$



Biasing Opamps to Have Stable g_m

- Transistor transconductances are the most important parameters. These must be stabilized over power-supply voltage, process, and T variations.
- Transistor transconductances can be matched to the conductance of a resistor: $(W/L)_{10} = (W/L)_{11}$, $g_{m13} = \sqrt{2\mu_n C_{ox}(W/L)_{13}I_{D13}}$

$$V_{GS13} = V_{GS15} + I_{D15}R_B, \quad I_{D13} = I_{D15}$$


$$\sqrt{\frac{2I_{D13}}{\mu_n C_{ox}(W/L)_{13}}} + V_{tn} = \sqrt{\frac{2I_{D13}}{\mu_n C_{ox}(W/L)_{15}}} + V_{tn} + I_{D13}R_B$$

$$\frac{2I_{D13}}{g_{m13}} \left[1 - \sqrt{\frac{(W/L)_{13}}{(W/L)_{15}}} \right] = I_{D13}R_B$$

$$g_{m13} = \frac{2 \left[1 - \sqrt{\frac{(W/L)_{13}}{(W/L)_{15}}} \right]}{R_B} = \frac{1}{R_B} \quad \text{for } (W/L)_{15} = 4(W/L)_{13}$$



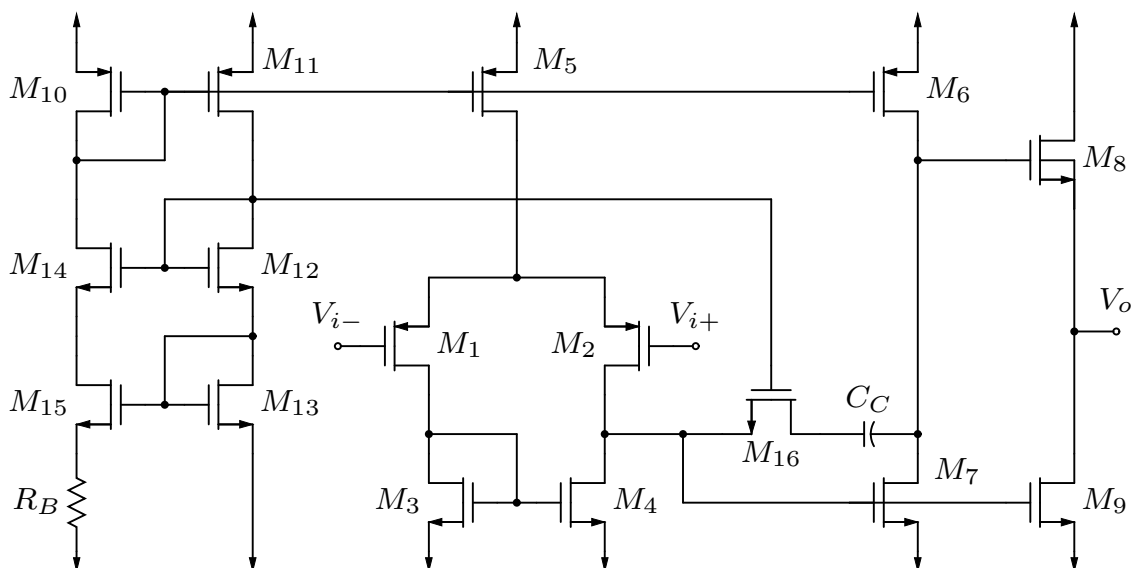- A two-stage CMOS opamp with a bias circuit that gives very predictable and stable transconductances.



- Stabilized transistor transconductances: $I_{Di} \propto I_{D13}$.

$$\frac{g_{mi}}{g_{m13}} = \frac{\sqrt{2\mu_i(W/L)_i I_{Di}}}{\sqrt{2\mu_n(W/L)_{13} I_{D13}}} = \sqrt{\frac{\mu_i (W/L)_i I_{Di}}{\mu_n (W/L)_{13} I_{D13}}} \propto \sqrt{\frac{(W/L)_i}{(W/L)_{13}}}$$

- Second-order effects.

- Body effect: modify the equation slightly.
- Transistor output impedance: use wide-swing cascode mirror.
- Mobility: proportional to $T^{-3/2}$, T increases 300 K to 373 K
 $\rightarrow V_{\text{eff}}$ increase by 27% for constant $g_{mi} = \mu_i C_{ox}(W/L)_i V_{\text{eff},i}$.

Tolerable design value : $0.2 \text{ V} \leq V_{\text{eff}} \leq 0.25 \text{ V}$ at 300 K

On-chip well or diffusion resistors with PTC: offset this effect.

- A start-up circuit for the bias circuit having positive feedback.



Homework

- Problems: 5.1, 5.2, 5.6, 5.8, 5.10, 5.12, 5.15.

- 그림 5.11의 CMOS 이단 연산 증폭기의 직류 이득, 단위 이득 주파수, 위상 여유, 입력 공통모드 범위, 슬루율, 오프셋 전압, 전력 소모, 출력 전압 범위, 그리고 안정 시간을 bsim3 모델을 사용하여 Spice로 구하라. 또한 다른 BSIM1이나 BSIM3 모델 두 가지에 대해서 특성들을 구하고, 세 가지 결과들에 대해 비교 분석하라.

CMOS 모델은 웹에서 탐색하거나 www.mosis.org에서 구할 수 있다. 그리고 회로 입력의 편의를 위해 회로 파일은 opa2.cir을 수정 보완하여 사용하라. (PSpice 9.1에서 BSIM3v3.1 모델의 LEVEL은 7이다.)

- 그림 5.11의 CMOS 이단 연산 증폭기를 Magic으로 레이아웃하라.

