

Sample/Holds, Voltage References, and Translinear Circuits

劉 尙 大 教授

전 자 공 학 부

Kyungpook National University

Integrated Systems Lab, Kyungpook National University



Sample and Holds

- ❑ A sample and hold is used to sample an analog signal and to store its value for length of time.
- ❑ Sample-and-hold circuits \simeq track-and-hold circuits, except for a few switched-capacitor S/H circuits without tracking phase.
- ❑ S/H circuits can greatly minimize errors due to slightly different delay times in the internal operation of data converters.
- ❑ A *sampling pedestal* or a *hold step*: This error is the difference between the hold voltage and the input voltage at the time of sampling (track \rightarrow hold). This error should be signal independent; otherwise it can introduce *nonlinear distortion*.

Integrated Systems Lab, Kyungpook National University




- ❑ The *signal isolation* between the input and the output of S/H circuits: In reality, there is always some signal feedthrough by parasitic capacitive coupling.
- ❑ The *speed* at which a S/H can track the input signal in sample mode. There are both small-signal and large-signal limitations due to 3-dB bandwidth and slew rate \rightarrow *acquisition time* (hold \rightarrow track).
- ❑ *Droop rate*: This error is a slow change in output voltage by leakage currents. In most CMOS designs, this can be ignored.
- ❑ *Aperture time* is delay time between hold command and real sample.
- ❑ *Aperture jitter* or *aperture time uncertainty*: the result of effective sampling time changing from one sampling instance to the next.
- ❑ Other parameters such as *dynamic range*, *linearity*, *gain*, PSRR, and *offset error* \rightarrow design principles for minimizing these errors.




A Popular Method for Testing S/Hs

- ❑ *Beat test*: This test consists of clocking the S/H at its maximum clock frequency and applying a sinusoidal input signal whose frequency is *slightly* different from the clock frequency. The output is demodulated to a low (*beat*) frequency Δf equal to the difference between the clock frequency and the signal frequency. This LF signal is then characterized by using a spectrum analyzer or by digitizing it using a high-accuracy ADC clocked at a frequency $\geq 2\Delta f$.

 

MOS Sample-and-Holds Basics

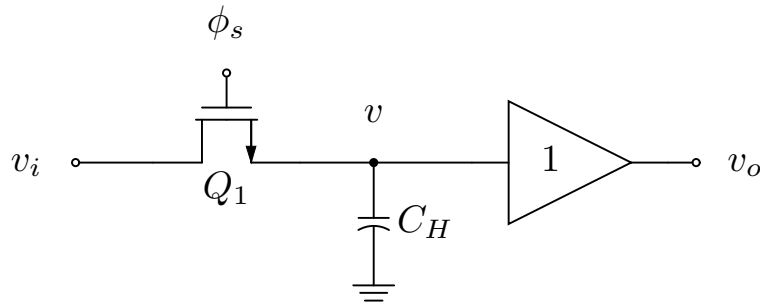- The simplest sample and hold: holding capacitor C_H .



- The charge injection: hold step $\Delta v \propto v_i$ (gain error), $V_{tn} = f(v_i)$ (signal-dependent error: distortion) ← body effect.

$$\Delta v = \frac{\Delta Q}{C_H} = -\frac{C_{ox}WL V_{eff}}{2C_H} = -\frac{C_{ox}WL(V_{DD} - V_{tn} - v_i)}{2C_H}$$


- The clock feedthrough: $\Delta v \neq f(v_i)$ (signal-independent offset),



power-supply noise on clock signal (poor PSRR).

$$\Delta v = -\frac{C_{ox}WL_{ov}(V_{DD} - V_{SS})}{C_H}$$

 
- A track and hold with a CMOS transmission gate: same size, assuming v_i in the middle region between V_{DD} and V_{SS} (same charges), fast and exactly complementary clock (same off times).




- A track and hold with a dummy switch: $W_2 = W_1/2$, fast clock waveform for good cancellation. The clock of Q_2 changes slightly



 after that of Q_1 to guarantee that the charge of Q_2 cannot escape through Q_1 . This technique can minimize Δv to less than about $1/5$




 □ Sampling jitter by clock waveforms having finite slopes: early, late.



A S/H Circuit with A Feedback Loop

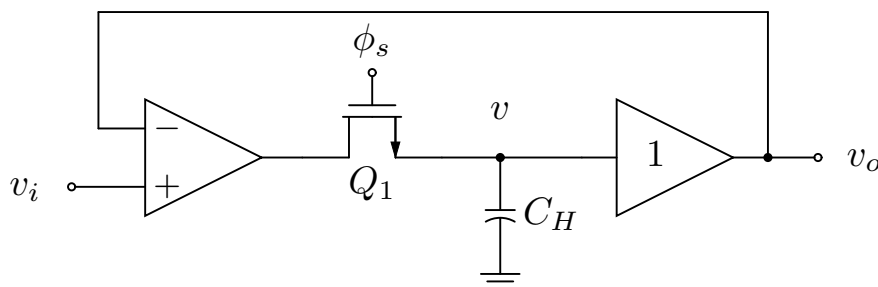□ A S/H circuit including an opamp in a feedback loop: to increase R_i




- V_{OS} of the opamp will remain, but V_{OS} of the buffer will not have an effect on $v_o = v_i + V_{OS}$. Errors due to charge injection, finite slopes.
- The speed can be seriously degraded due to frequency compensation. Another source of speed degradation is the slewing time it takes for the opamp to return from saturation (hold mode) to track mode.



A S/H Circuit with Two Additional Switches

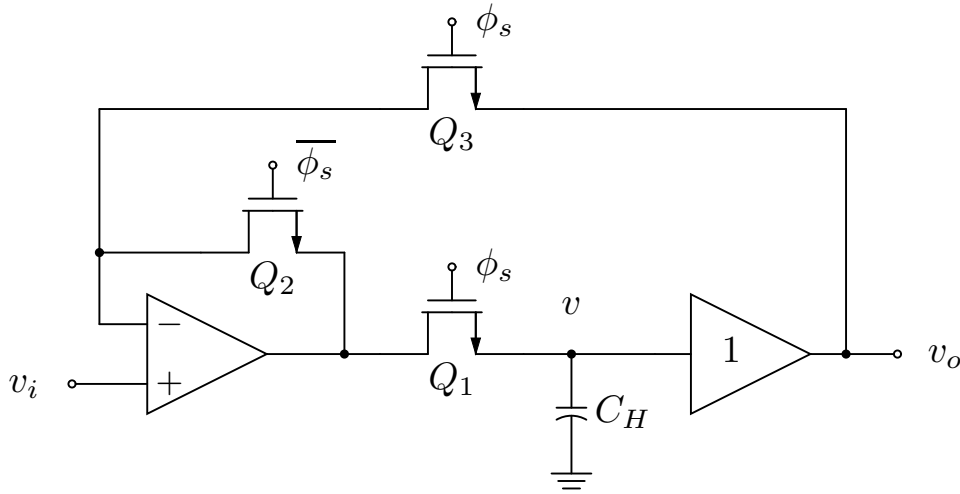- A S/H circuit adding two switches to minimize slewing time.




- This S/H still has errors due to charge injection from Q_1 and finite clock rise and fall times.



An Improved S/H Circuit

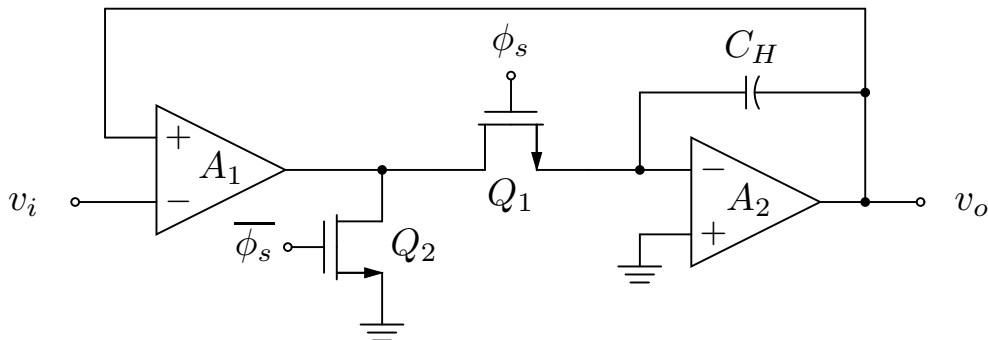- Signal independent error, slewing and signal feedthrough ↓ by Q_2 , but speed ↓ due to frequency compensation of two opamps.




- The voltages on both sides of Q_1 are nearly signal independent as virtual ground. Thus the charge injection due to Q_1 will cause just a dc offset but no distortion. In addition, the sampling time will not change due to the finite slopes of clock waveform.



A S/H with Clock-Feedthrough Cancellation

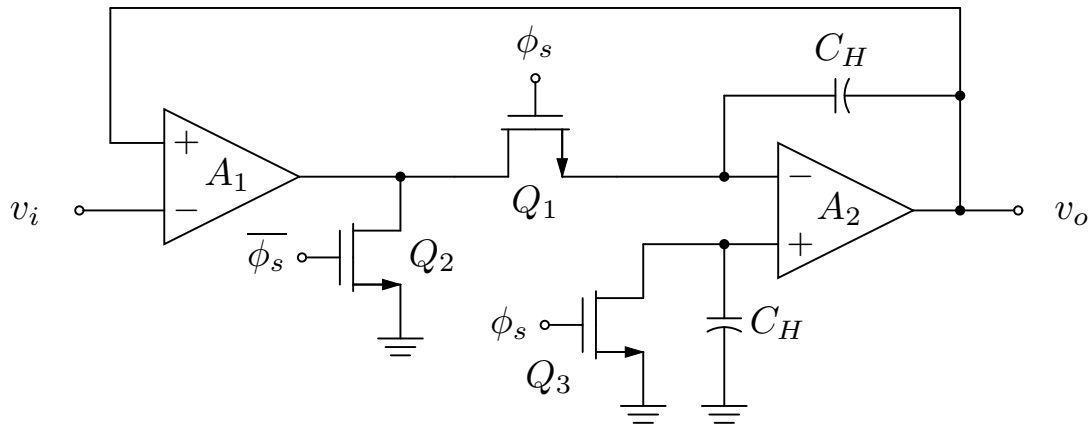- A S/H circuit with additional circuitry to minimize the dc offset.




- The common-mode rejection of opamp will eliminate the effects of charge injection on the output voltage. This configuration using fully differential design is a reasonable choice for many applications.



Other Examples of CMOS S/H Circuits

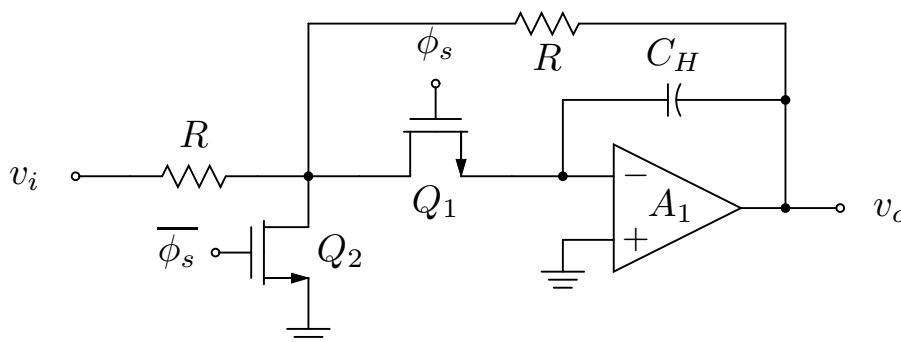- The choice for a S/H is dependent on application and technology.
- An inverting track and hold: clock feedthrough and sampling time are signal independent, track mode (LPF) $H(s) = -1/(1 + sRC_H)$.




- A small capacitor C_C can be included in parallel to the input resistor to improve the speed (APF) $\rightarrow H(s) = -(1 + sRC_C)/(1 + sRC_H)$.



A S/H with Clock-Feedthrough Cancellation

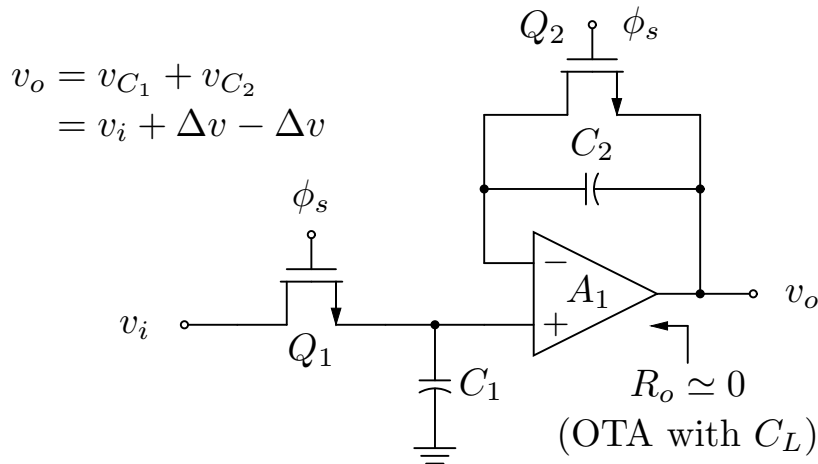- A simple noninverting S/H circuit for high-speed applications.




- The charge injection of Q_1 will be matched by the charge injection of Q_2 since both are at the same voltage and have the same clock.



A S/H with Miller Holding Capacitor

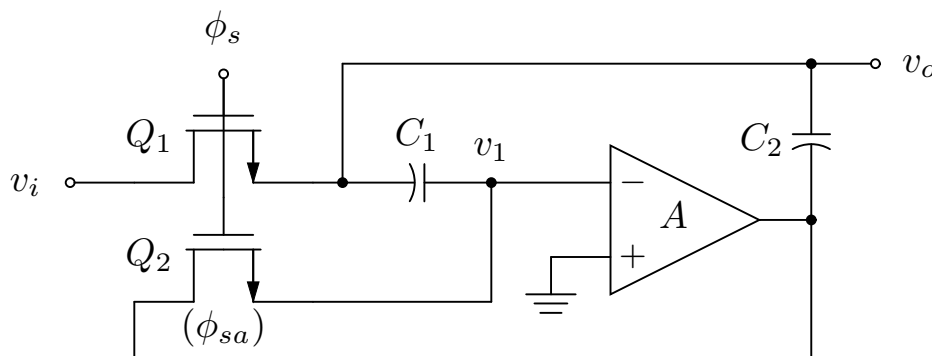- An open-loop S/H circuit with large Miller C_H : smaller capacitances, switches, and voltage changes at the output \rightarrow very high speed.



- The effective holding capacitance at the inverting input of opamp.

$$C_H = (1 + A)C_1C_2 / (C_1 + C_2)$$



- Reduction of charge injection error by Miller effect.

$$\Delta v_{o1} \simeq \Delta Q_1 / AC_2, \quad \Delta v_{o2} \simeq \Delta Q_2 / C_1 \text{ (dc offset)}$$

- Charge injection error by Q_1 : C_i = input capacitance of opamp.

$$\Delta Q_1 = \Delta Q_{C_1} + \Delta Q_{C_2}, \quad \Delta Q_{C_1} = \Delta Q_{C_i}$$

$$\Delta Q_{C_1} = (\Delta v_{o1} - \Delta v_1)C_1 = \Delta v_1 C_i, \quad \therefore \Delta v_1 = \frac{C_1 \Delta v_{o1}}{C_1 + C_i}$$

$$\Delta Q_{C_1} = \Delta v_1 C_i = \frac{C_i C_1}{C_1 + C_i} \Delta v_{o1}$$

$$\Delta Q_{C_2} = [\Delta v_{o1} - (-A \Delta v_1)]C_2 = \frac{(C_1 + C_i + AC_1)C_2}{C_1 + C_i} \Delta v_{o1}$$


$$\Delta Q_1 = \frac{(C_1 + C_2)C_i + (A + 1)C_1 C_2}{C_1 + C_i} \Delta v_{o1}$$

$$\Delta v_{o1} = \frac{(C_1 + C_i) \Delta Q_1}{(C_1 + C_2)C_i + (A + 1)C_1 C_2} \simeq \frac{\Delta Q_1}{AC_2}$$




Switched-Capacitor S/H Circuits

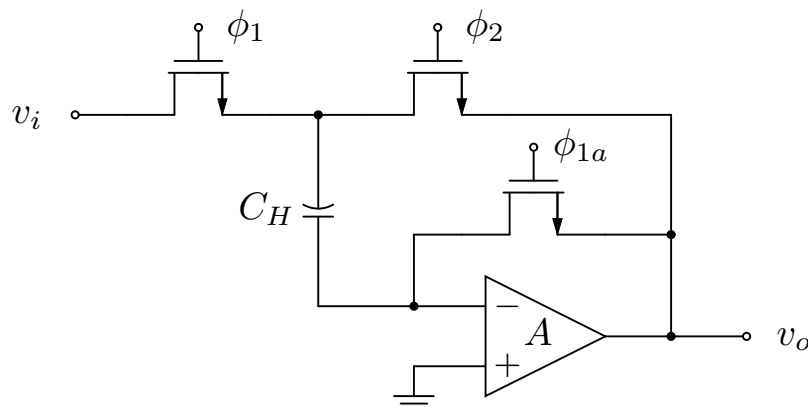
- Quite accurate but not necessarily fast → low frequency circuit.
- A simple SC S/H: During ϕ_1 , C_H is charged up to $v_i - V_{OS}$ and $v_o = V_{OS}$ (not track). During ϕ_2 , v_o is equal to $v_i - V_{OS} + V_{OS} = v_i$, $\Delta v \neq 0$. Large changes of the opamp output voltage → low speed.



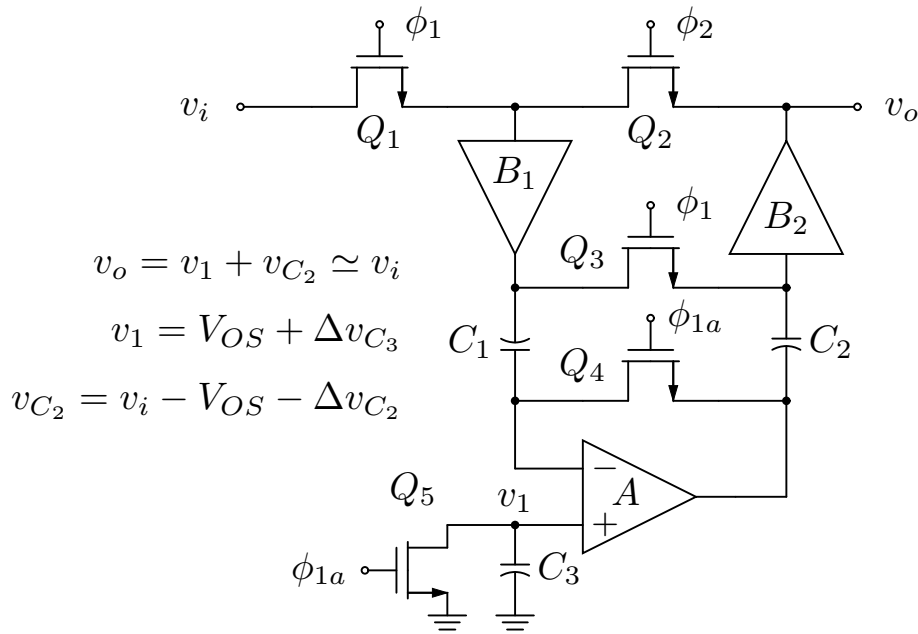- A recycling SC S/H to improve accuracy: charge injections (Q_4, Q_5 : dc offset, cancelled by CMR), (Q_3 : signal dependent but minimized by Miller effect), (Q_1, Q_2 : no effect due to B_1 and B_2).



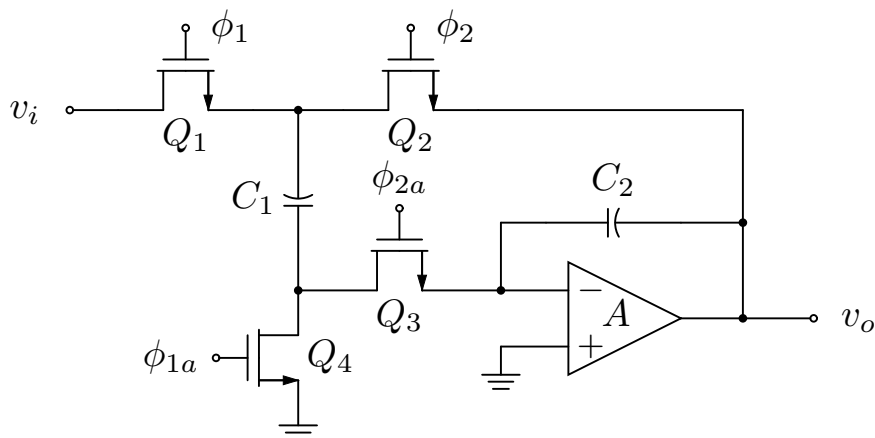- A switched-capacitor S/H with a low-pass filter: signal conversion from sampled-data domain to continuous-time domain, the charge of C_1 is shared with the charge of $C_2 \rightarrow$ LPF, high-Q audio DAC.



- Errors: dc offset (Q_3, Q_4), signal dependent (Q_2 : reduced by Miller effect), can be minimized by cancellation or differential architecture.
- Unlike previous circuits, V_{OS} is not eliminated but v_o is always valid.



- Transfer function by discrete-time analysis.

$$v_i(n-1)C_1 + v_o(n-1)C_2 = v_o(n)(C_1 + C_2)$$

$$z^{-1}V_i(z)C_1 + z^{-1}V_o(z)C_2 = V_o(z)(C_1 + C_2)$$

$$H(z) = \frac{V_o(z)}{V_i(z)} = \frac{C_1}{(C_1 + C_2)z - C_2}, \quad z_p = \frac{C_2}{C_1 + C_2}$$

- Cutoff frequency of the switched-capacitor LPF: $f \ll f_s = 1/T$

$$z = e^{sT} \simeq 1 + sT \quad \text{for } |sT| \ll 1$$

$$H_c(s) = H(z)|_{z=1+sT} = \frac{C_1}{C_1 + s(C_1 + C_2)/f_s} = \frac{1}{1 + s/\omega_p}$$

$$f_p = \frac{f_s C_1}{2\pi(C_1 + C_2)} \simeq \frac{f_s C_1}{2\pi C_2} \quad (C_2 \gg C_1)$$



Bandgap Voltage Reference Basics

- The approaches to realize voltage references in integrated circuits.

- (1) Making use of a Zener diode.

Not popular because breakdown voltage $>$ power supply voltage.

- (2) Making use of the difference in V_t between efet and dfet.


Cannot be used in most CMOS circuits because dfet is not available, process sensitivity of reference voltage due to dependence of V_t on doping concentration.

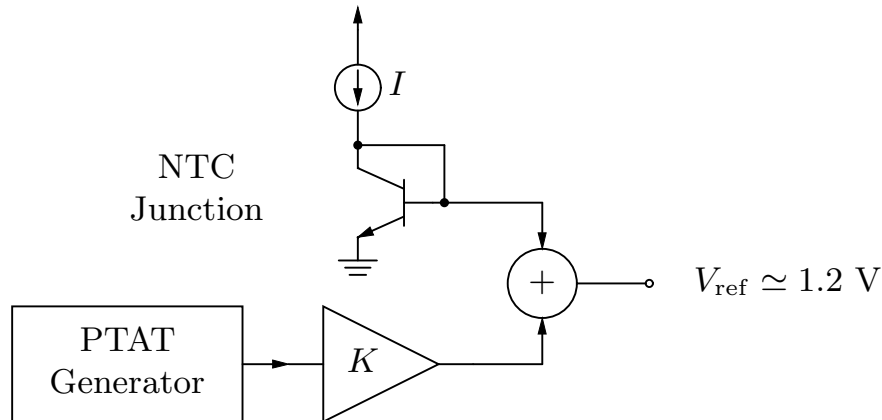- (3) Cancelling NTC of a pn junction with PTC (positive temperature coefficient) of a PTAT (proportional to absolute temperature) circuit. Bandgap voltage reference is the most popular for both bipolar and CMOS technologies.



Bandgap Voltage Reference

- A simplified circuit of a bandgap voltage reference.



- Bipolar transistor equation.

$$I_C = I_S e^{V_{BE}/V_T} \equiv I_S e^{qV_{BE}/kT} \leftarrow \text{strong dependence on } T$$



- Temperature dependence of V_{BE} : $TC \simeq -2 \text{ mV/K}$, $\eta \equiv 4 - n \simeq 2.3$, $n = \text{exponential TC of mobility}$, $T_r = \text{reference temperature}$.

$$V_{BE}(T) = V_G(T) - \left(\frac{T}{T_r}\right) V_G(T_r) + \left(\frac{T}{T_r}\right) V_{BE}(T_r) - \eta \left(\frac{kT}{q}\right) \ln\left(\frac{T}{T_r}\right) + \left(\frac{kT}{q}\right) \ln\left[\frac{I_C(T)}{I_C(T_r)}\right] \leftarrow \begin{matrix} \text{design} \\ I_C \propto T \end{matrix}$$

- Temperature dependence of silicon bandgap voltage.

$$V_G(T) = a - bT - cT^2, \quad \text{error} < 0.2 \text{ mV}$$

$$\left. \begin{matrix} a = 1.1785 \text{ V} \\ b = 9.025 \times 10^{-5} \text{ V/K} \\ c = 3.05 \times 10^{-7} \text{ V/K}^2 \end{matrix} \right\} \text{ for } 150 \text{ K} < T < 300 \text{ K}$$



$$\left. \begin{aligned} a &= 1.20595 \text{ V} \\ b &= 2.7325 \times 10^{-4} \text{ V/K} \\ c &= 0 \text{ V/K}^2 \end{aligned} \right\} \text{ for } 300 \text{ K} \leq T < 400 \text{ K}$$

- Generation of PTAT voltage: $TC \simeq 0.198 \text{ mV/K}$, the difference in two base-emitter junction voltages, quite accurate even if $I_C = f(T)$.


$$\Delta V_{BE} = V_{BE1} - V_{BE2} = \frac{kT}{q} \ln \left(\frac{I_{C1} I_{S2}}{I_{C2} I_{S1}} \right) \equiv V_T \ln \left(\frac{J_1}{J_2} \right)$$

- Bandgap voltage reference = $V_{BE}(T) + K \Delta V_{BE}(T) \simeq 1.235 \text{ V}$.


$$\begin{aligned} V_{\text{ref}} &= V_G(T) - \left(\frac{T}{T_r} \right) V_G(T_r) + \left(\frac{T}{T_r} \right) V_{BE}(T_r) \\ &\quad - (\eta - 1) \left(\frac{kT}{q} \right) \ln \left(\frac{T}{T_r} \right) + K \left(\frac{kT}{q} \right) \ln \left(\frac{J_1}{J_2} \right) \end{aligned}$$



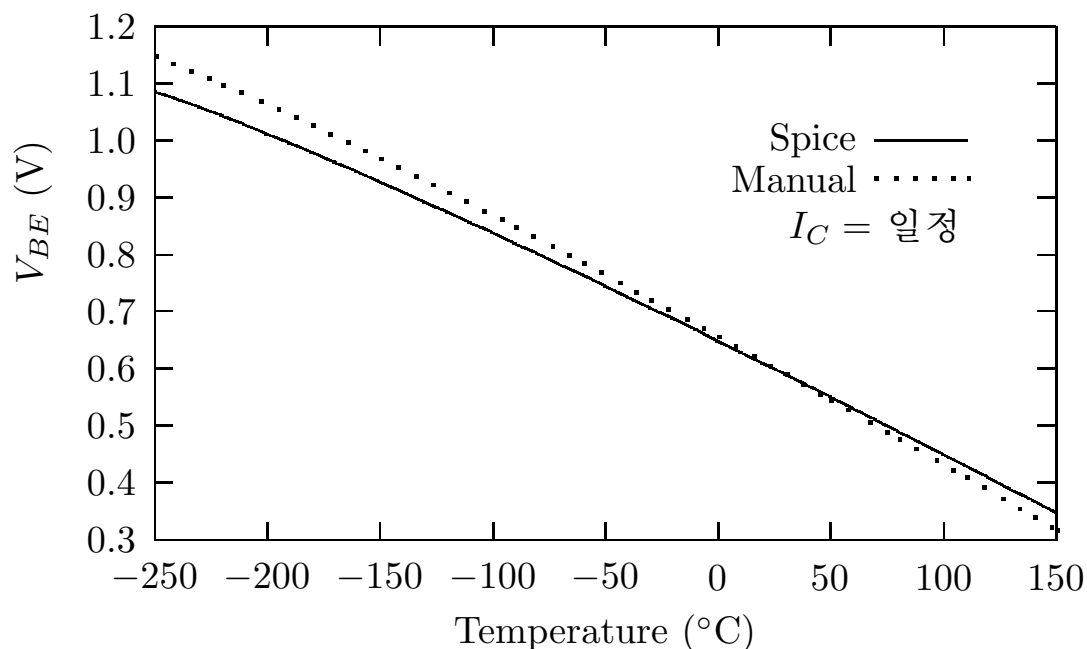V_{BE} Plot by Simulation and Calculation




Ideal Bandgap Reference Voltage

 

A Bipolar Bandgap Voltage Reference

□ Reference voltage: $I_{C1} = I_{C2} \rightarrow I_{E1} = I_{E2} = \Delta V_{BE}/R_2$.
 
$$V_{ref} = V_{BE1} + V_{R1} = V_{BE1} + 2R_1 I_{E2} = V_{BE1} + \frac{2R_1}{R_2} \Delta V_{BE}$$




$$A_{E2} = 8A_{E1}$$

$$\Delta V_{BE} = V_T \ln \left(\frac{A_{E2}}{A_{E1}} \right)$$



Bipolar Transistors in CMOS Processes

 
- *Well transistors*: vertical bipolar transistors use wells as bases and the substrate as collectors, reasonable current gain but large base resistance $\rightarrow I_C < 0.1 \text{ mA}$, *n-well* process is the most common CMOS process (*npn* with grounded collector).



A CMOS Bandgap Voltage Reference

- Bandgap voltage reference in an *n-well* CMOS process.
 
$$V_{\text{ref}} = V_{EB1} + V_{R1} = V_{EB1} + V_{R2} = V_{EB1} + \frac{R_2}{R_3} \Delta V_{EB}$$




$$A_{E1} = A_{E2}$$


$$\Delta V_{EB} = V_T \ln \left(\frac{R_2}{R_1} \right)$$



 
□ Operating points of the bandgap-reference circuit.



A CMOS Bandgap Reference Circuit

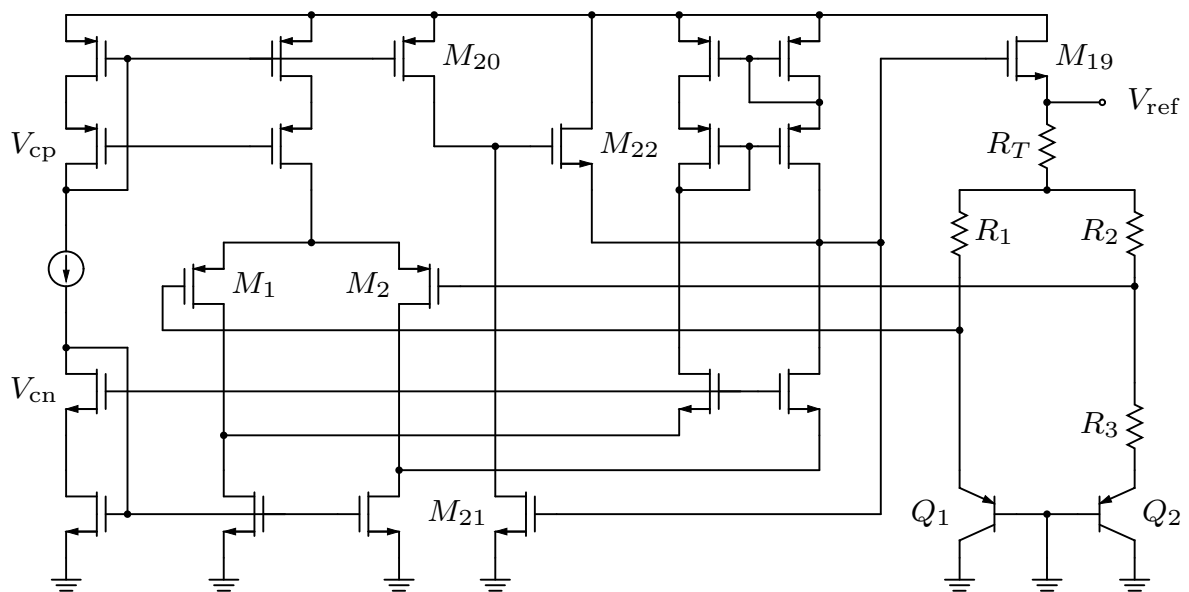

 □ Temperature variations of the reference voltage V_{ref} : 15 ppm/°C.



Performances of CMOS Bandgap Reference


Output voltage	1.168 V
Temperature coefficient	15 ppm/°C
Line regulation	1.29 mV/V
Minimum supply voltage	3.7 V
Power-supply rejection ratio	58 dB
Power dissipation @ $V_{DD} = 5\text{ V}$	0.8 mW

□ Error sources: temco of well resistors ($\eta = 2.2$), offset voltage $V_{OS}(T)$, second-order effects \rightarrow SC amplifier, *curvature correction* method.

$$R(T) = R_0 \frac{T^\eta}{T_0^\eta}, \quad \text{TC}_{\text{error}} \simeq 26 \text{ ppm}/^\circ\text{C} \text{ for } 1 \text{ mV offset}$$



An SC-Based Bandgap Reference

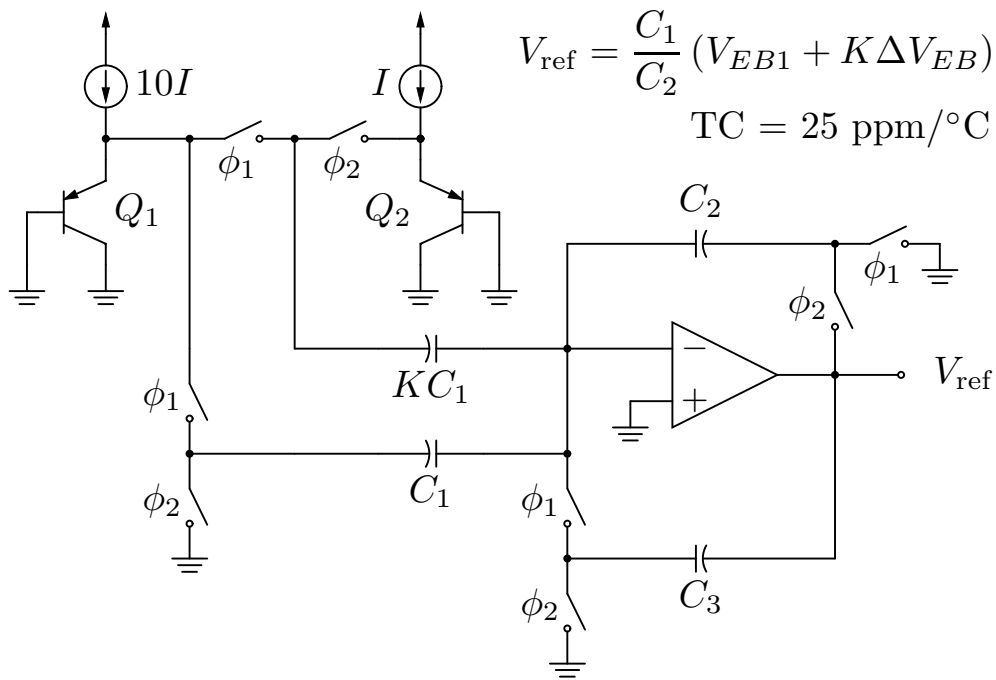

Curvature-Corrected Bandgap Reference

- First-order compensated BGR.

$$\text{TC} \equiv \frac{1}{V_{\text{ref}}} \left(\frac{V_{\text{max}} - V_{\text{min}}}{T_{\text{max}} - T_{\text{min}}} \right) = 20 \sim 60 \text{ ppm}/^\circ\text{C}$$

- Curvature-compensation concept: PTAT^2 , $\beta(T)$, ΔV_{BE} for transistors biased at a constant and a PTAT current.


$$V_{\text{ref}} = V_{BE} + K_1 V_T + K_2 H(T)$$

- Exponential curvature-compensated BGR: ΔE_G (bandgap narrowing factor) $\simeq 63.9 \text{ meV}$.

$$\beta(T) = \beta_\infty \exp \left(-\frac{\Delta E_G}{kT} \right)$$



Curvature-Corrected Reference Voltage

 

Translinear Gain Cell

- Gilbert gain cell: pn junction loads + differential pair, current amplifier, variable gain for continuous-time filters, voltage-controlled amplifiers, analog multipliers (translinear or Gilbert multipliers).
- Voltage difference between emitters: Q_1 and Q_2 matched, $i_B \approx 0$.

$$\Delta V \equiv v_{E2} - v_{E1} = V_T \ln \left(\frac{I_1 + i_i}{I_1 - i_i} \right) \leftarrow V_{BE} = V_T \ln \frac{I_C}{I_S}$$


- Output current: gain and linearity are not dependent on β or I_S .

$$i_{C3} = \frac{2\alpha I_2}{1 + e^{-\Delta V/V_T}} = \frac{2\alpha I_2}{1 + \left(\frac{I_1 - i_i}{I_1 + i_i} \right)} = \alpha I_2 + \alpha \frac{I_2}{I_1} i_i \simeq I_2 + \frac{I_2}{I_1} i_i$$

$$i_{C4} \simeq I_2 - \frac{I_2}{I_1} i_i, \quad \therefore i_o = i_{C3} - I_2 = I_2 - i_{C4} \simeq \frac{I_2}{I_1} i_i$$



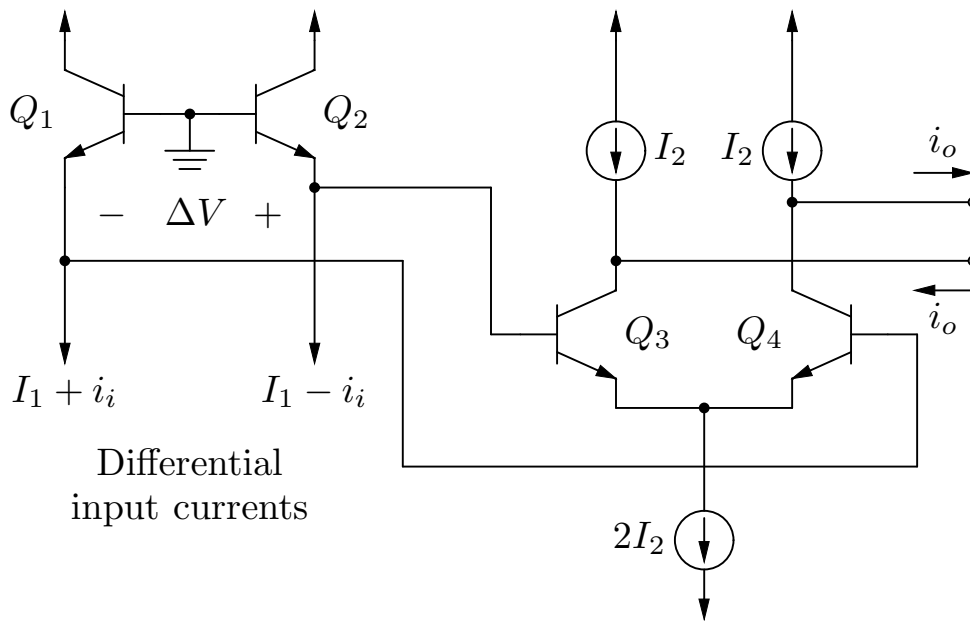□ A translinear gain cell: $i_o \times I_1 = I_2 \times i_i$, analog multiplier: $i_o I_1 = i_1 i_2$.



Homework

- Problems: 8.3, 8.4, 8.6, 8.9, 8.13.
- Describe the operation principle of the bandgap reference [1].

References

- [1] H. Banba, H. Shiga, A. Umezawa, T. Miyaba, T. Tanzawa, S. Atsumi, and K. Sakui, "A CMOS bandgap reference circuit with sub-1-V operation" *IEEE J. of Solid-State Circuits*, vol. 34, no. 5, pp. 670–674, 1999.
- [2] W. T. Holman, "New temperature compensation technique for bandgap voltage references", *IEEE International Symposium on Circuits and Systems*, vol. 1, pp. 358–388, 1996.
- [3] I. Lee, G. Kim, and W. Kim, "Exponential curvature-compensated BiCMOS bandgap references", *IEEE J. of Solid-State Circuits*, vol. 29, no. 11, pp. 1396–1403, 1994.

